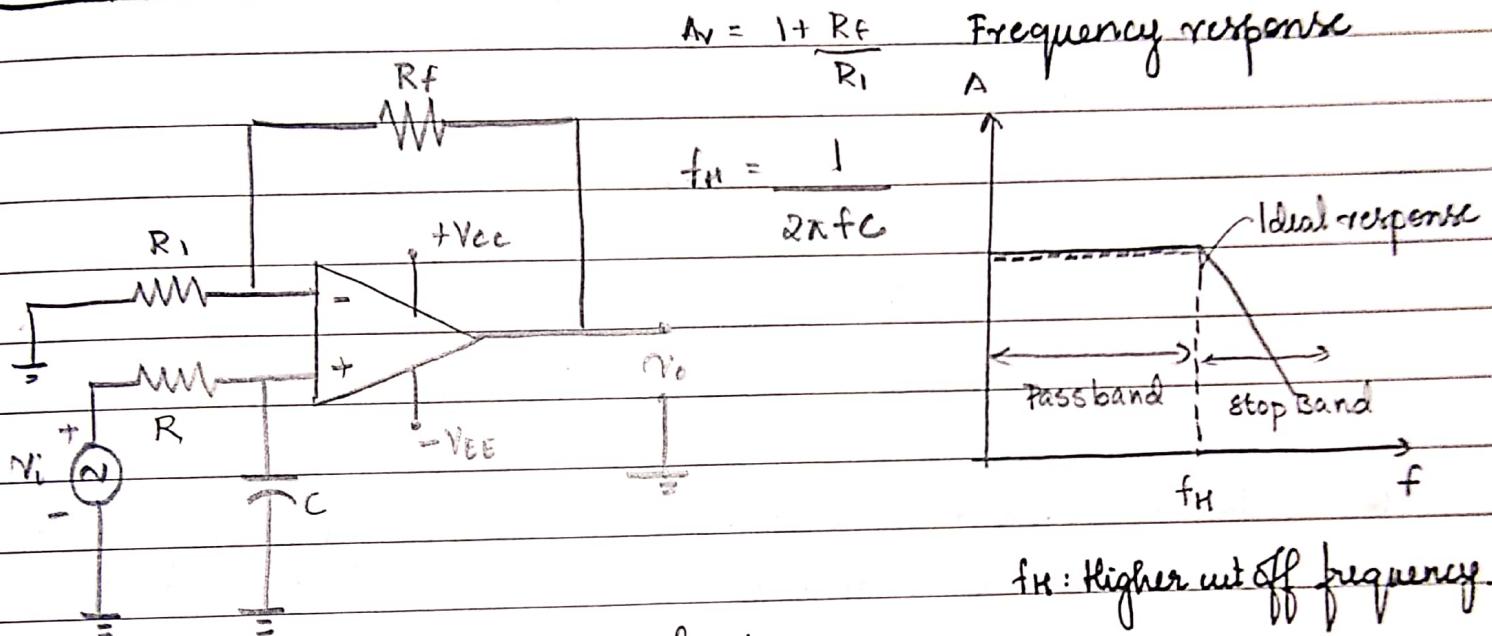


Low Pass Filter:

$f_H$ : Higher cut off frequency

A low pass filter has a constant gain from 0Hz to a high cut off frequency  $f_H$ . A low pass filter allows frequency upto  $f_H$  and then attenuates the higher frequency after  $f_H$  the gain is decreasing with the increase in input frequency. Bandwidth is equal to  $f_H$ .

Frequencies between 0Hz to  $f_H$  : pass band frequencies  
 Frequencies which are above  $f_H$  are attenuated : stop band frequencies.

Q1: Design a low pass filter at a cut off frequency  $f_H = 10\text{ kHz}$  and pass band gain of 2.

Sol: Given:  $A_P = 2 \quad f_H = 10\text{ kHz}$

$$f_H = \frac{1}{2\pi RC}$$

$$A_P = 1 + \frac{R_f}{R_1}$$

$$RC = \frac{1}{2\pi(10k)}$$

$$\mathcal{D} = 1 + \frac{R_f}{R_1}$$

Assuming  $C = 0.01\mu\text{F}$

$$R = \frac{1}{2\pi(10k)(0.01\mu)}$$


$$\frac{R_f}{R_1} = 1$$

$$\Rightarrow R_f = R_1$$

$$R = 1.6\text{k}\Omega$$

Assuming  $R_f = 10\text{k}\Omega$

$$\therefore R_1 = 10\text{k}\Omega$$

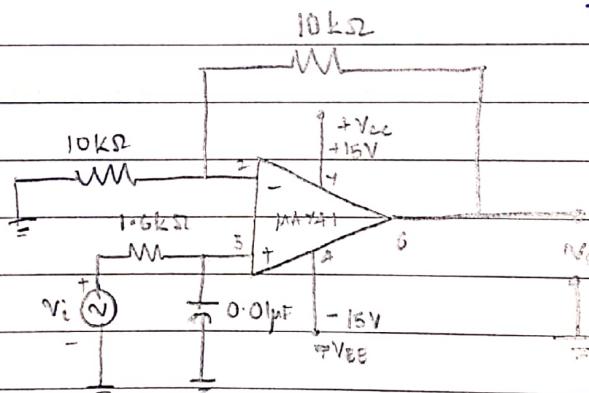

Q2: Design a low pass filter at a cut off frequency of  $15.9\text{ kHz}$  with a pass band gain of 1.5.

Sol:  $f_H = \frac{1}{2\pi RC}$

$$A = 1.5 = 1 + \frac{R_f}{R_1}$$

Assuming  $C = 0.01\mu\text{F}$


$$R = \frac{1}{2\pi(15.9k)(0.01\mu)}$$

$$\Rightarrow R_f = 0.5R_1$$


$$R = 1\text{k}\Omega$$

Assuming  $R_f = 10\text{k}\Omega$

$$R_1 = 20\text{k}\Omega$$

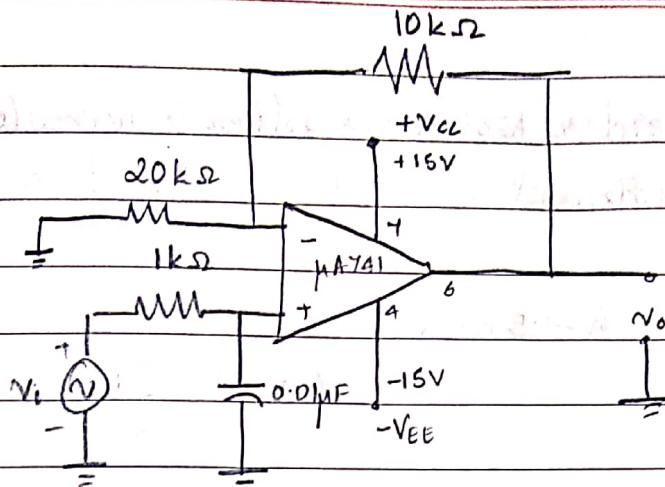

\* High Pass Filter:

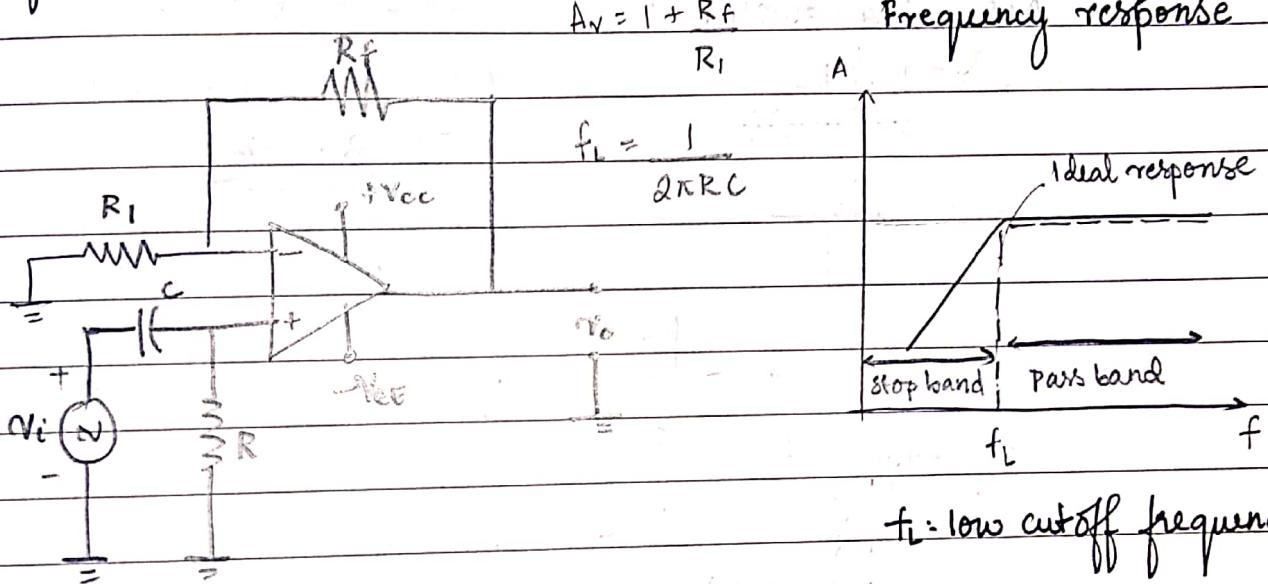

A high pass filter has a constant gain from low cut off frequency and above. A high pass filter attenuates frequencies upto  $f_L$  and then allows frequency above  $f_L$ .

From 0Hz to  $f_L$  the gain increases with increase in input frequency.

Frequencies between 0Hz to  $f_L$  : stop band frequencies as they are attenuated and frequencies above  $f_L$  : pass band frequencies.

Q1: Design a first order high pass filter to have lower cut off frequency of 1.5 kHz and a pass band gain of 1.5.

Sol: Given:  $f_L = 1.5 \text{ kHz}$   $A = 1.5$

$$f_L = \frac{1}{2\pi RC}$$

$$A = 1 + \frac{R_f}{R_1}$$

$$RC = \frac{1}{2\pi(1.5k)}$$

$$1.5 = 1 + \frac{R_f}{R_1}$$


Assuming  $C = 0.01 \mu\text{F}$

$$R = 10.6 \text{ k}\Omega$$

$$R_f = 0.5 R_1$$

Assuming  $R_f = 10 \text{ k}\Omega$

$$R_1 = 20 \text{ k}\Omega$$

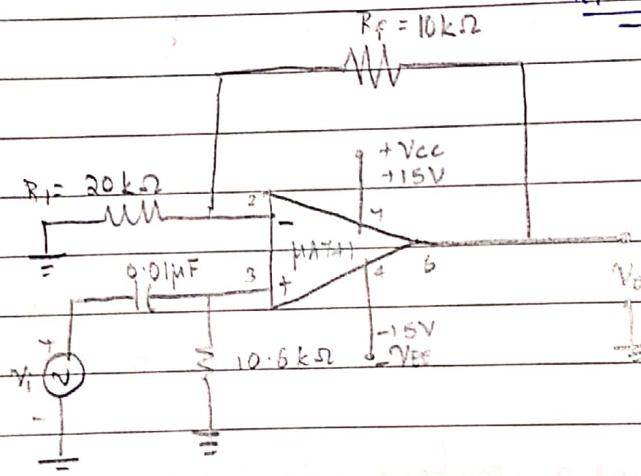

#### \* Differentiator and Integrator:

→ Design steps for differentiator and integrator:

Select  $f_a$  equal to highest frequency of the input signal to be differentiated. Then assuming the value of  $C_1 < 1 \mu\text{F}$ .

Calculate the value of  $R_f$

$$f_a = \frac{1}{2\pi R_f C_f}$$

$$f_b = \frac{1}{2\pi R_1 C_1}$$

$$R_1 C_1 = R_f C_f$$

Choose  $f_b = 10 f_a$  or  $f_b = 20 f_a$  and calculate  $R_1$  and  $f_f$ . (In most of the wave shaping circuits and FM modulators we use integrator and differentiator.)

classmate

Date \_\_\_\_\_  
Page \_\_\_\_\_

## Differentiator:

The circuit performs the mathematical operation of differentiation i.e., the output waveform is the derivative of the input waveform. The differentiator is constructed by replacing the input resistance  $R_i$  of inverting amplifier by a capacitor  $C_1$ .

Due to virtual ground

$$V_x = 0$$


Applying KCL

$$I_i = I_f$$

$$C_1 \frac{d[V_i - V_x]}{dt} = \frac{V_x - V_o}{R_f}$$

$$C_1 \frac{dV_i}{dt} = -\frac{V_o}{R_f}$$

$$V_o = -R_f C_1 \frac{dV_i}{dt}$$

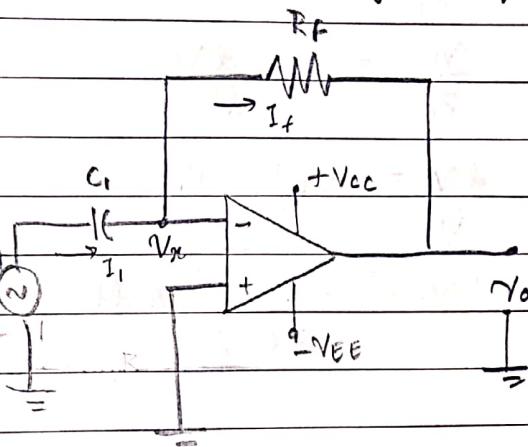

## Differentiator

Input:

sine

triangular

Output:

sine

square wave

## Integrator:

A circuit in which the output voltage waveform is the integral of the input voltage waveform is the integrator or the integration amplifier. Such a circuit is obtained by using a basic inverting amplifier configuration if the feedback resistor  $R_f$  is replaced by a feedback capacitor  $C_f$ .

Due to virtual ground

$$V_A = 0$$

Applying KVL

$$I_1 = I_f$$


$$\frac{V_i - V_A}{R_1} = C \frac{d}{dt} [V_A - V_o]$$

$$R_1$$

$$\frac{V_i}{R_1} = -C \frac{d V_o}{dt}$$

$$\frac{d V_o}{dt} = -\frac{1}{R C} V_i$$

$$V_o = -\frac{1}{R C} \int_0^t V_i dt$$

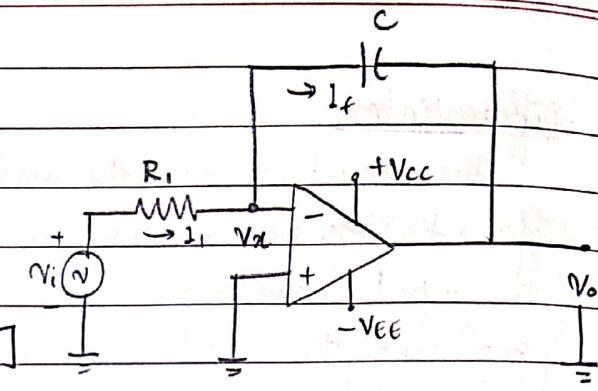

Integrator:

Input	Output
sine	cosine
square	triangular

- Q1: a. Design a differentiator to differentiate an input signal that varies in frequency from 10Hz to about 1kHz.  
 b. If a sine wave of 1V peak at 1000Hz is applied to the differentiator of part a, then draw the output waveform.

sol: Given:  $f_a = 1\text{ kHz}$   $f_b = 10\text{ Hz}$

$$f_a = \frac{1}{2\pi R_f C_f}$$

$$\Rightarrow R_f = \frac{1}{2\pi(1\text{k})(0.01\mu)}$$

$$R_f = 1.59\text{ k}\Omega$$

$$f_b = 20f_a$$


$$f_b = 20(1\text{k})$$

$$f_b = 20\text{ kHz}$$

Assuming  $C_f < 1\mu\text{F}$

$$1.59\text{ k}\Omega$$

1M

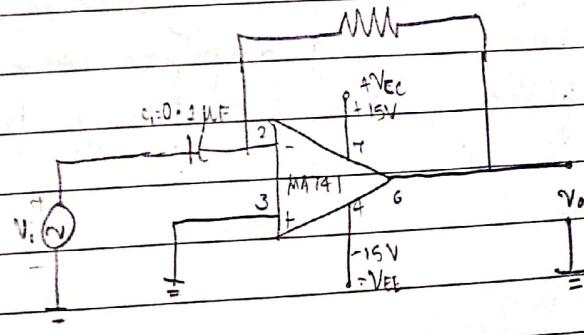

$$f_b = \frac{1}{2\pi R_1 C_1}$$

$$20k = \frac{1}{2\pi R_1 (0.1\mu F)} \quad \text{assuming } C_1 < 1\mu F$$

$$\underline{R_1 = 79.57\Omega}$$


b.  $V_o = -R_f C_1 \frac{dV_i}{dt}$

$$V_o = -(1.59k)(0.1\mu) \frac{d}{dt} (\sin \omega t)$$

$$V_o = -159 \times 10^{-6} \omega \cos \omega t$$

$$V_o = -159 \times 10^{-6} (2\pi(1000)) \cos \omega t$$
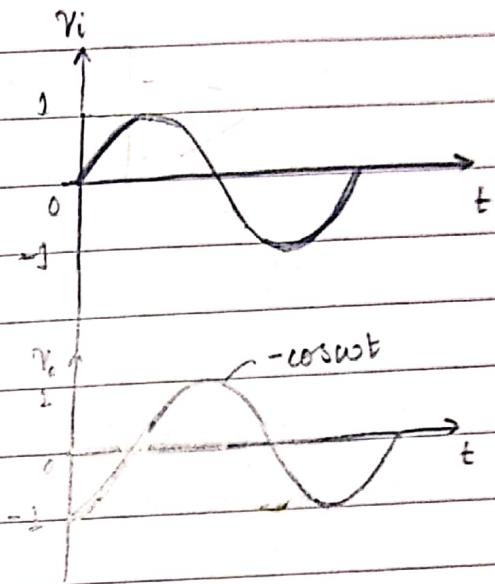
$$\underline{V_o = -0.999 \cos \omega t}$$



Q2: Design a differentiator using op-amp to differentiate an input signal with  $f_{max} = 200\text{Hz}$ . Also draw the output waveform for a sine wave input of  $1V_p$  at  $200\text{Hz}$ .

sol:  $f_a = 200\text{Hz}$

Assume:  $C_f = 0.1\mu F$

$$f_a = \frac{1}{2\pi R_f C_f} \Rightarrow R_f = \frac{1}{2\pi(0.1\mu F)(200)}$$

$$\therefore \underline{R_f = 7.95\text{k}\Omega}$$

$$f_b = 10f_a = 2000\text{Hz}$$

$$f_b = \frac{1}{2\pi R_1 C_1} \Rightarrow R_1 = \frac{1}{2\pi(2000)(0.1\mu)}$$

$$\therefore \underline{R_1 = 0.795\text{k}\Omega}$$

$$V_i = 1 \sin(2\pi \times 200)t$$


$$V_o = -R_f C_1 \frac{dV_i}{dt}$$

$$V_o = -(7.95k)(0.1\mu) \frac{d}{dt} \sin(2\pi \times 200)t$$

$$V_o = -7.95 \times 10^{-1} \cos(2\pi 200t) \times 2\pi (200)$$

$$V_o = -0.999 \cos(2\pi 200t)$$

$$V_o \approx -1 \cos(2\pi 200t)$$

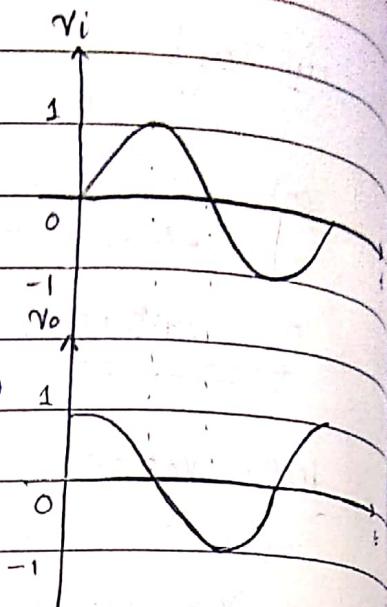

Q3: Assuming \$R\_f = 100k\Omega\$ and \$R\_i = 10k\Omega\$ and \$C\_f = 10nF\$ in a practical integrator circuit, determine the lower frequency limit of integrator and output response for the sine wave input.

Sol: \$R\_i = 10k\Omega\$ \$R\_f = 100k\Omega\$ \$C\_f = 10nF\$

$$f_a = \frac{1}{2\pi R_f C_f}$$

$$\Rightarrow f_a = \frac{1}{2\pi(100k)(10n)} = 159 \text{ Hz}$$


For an input voltage of 1Vp and 2.5kHz

$$V_o = \frac{-1}{R_i C_f} \int V_i(t) dt$$

$$V_o = \frac{-1}{(10k)(10n)} \int \sin 2\pi (2.5k)t dt$$

$$V_o = -10000 \frac{[-\cos 2\pi (2.5k)t]}{2\pi (2.5k)}$$

$$V_o = 0.636 \cos 2\pi (2.5k)t$$

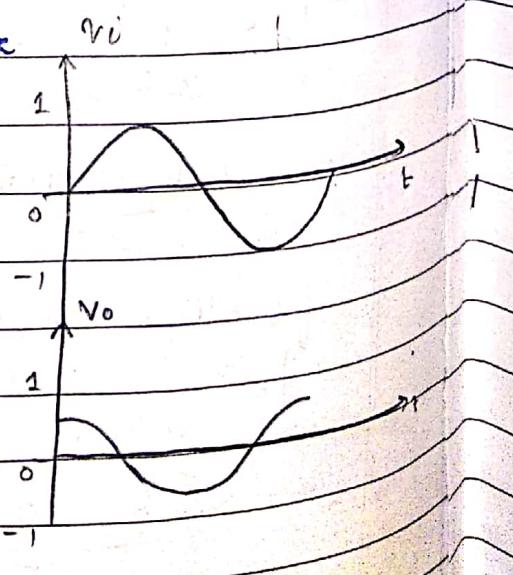

\* Summing, Scaling and averaging amplifiers using op-amp:  
 Different configurations.

- Inverting configuration

- Noninverting configuration

- Differential configuration.

\* Inverting configuration:

Due to virtual ground

$$V_1 = V_2 = 0$$

$$\Rightarrow I_{B1} = I_{B2} = 0$$


$$I_{B1} = I_{B2} = I_B$$

Applying KCL at  $V_2$

$$I_a + I_b + I_c = I_f + I_B$$

$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = -\frac{V_o}{R_f}$$
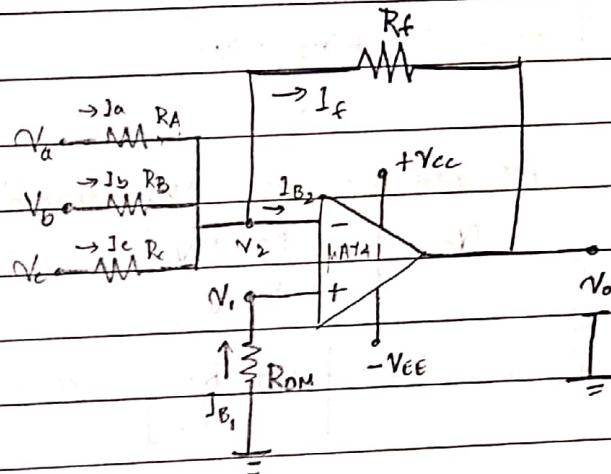
$$\Rightarrow V_o = - \left[ \frac{R_f}{R_a} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_c \right]$$



a. Summing amplifier:

If  $R_a = R_b = R_c = R$ , then

$$V_o = -\frac{R_f}{R} [V_a + V_b + V_c]$$

If gain is 1 then  $V_o = -[V_a + V_b + V_c]$

b. Scaling or Weighted Amplifier:

$$\frac{R_f}{R_a} \neq \frac{R_f}{R_b} \neq \frac{R_f}{R_c}$$

$$V_o = - \left[ \frac{R_f}{R_a} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_c \right]$$

c. Averaging amplifier:

If  $R_a = R_b = R_c = R$  and gain  $\frac{R_f}{R} = \frac{1}{n}$  where  $n$  is number of inputs.

$$V_o = -\frac{1}{n} [V_a + V_b + V_c]$$

\* NON INVERTING CONFIGURATION:


Here  $R_a = R_b = R_c = R$

By superposition principle

$$V_o = \frac{R/2}{R+R/2} V_a + \frac{R/2}{R+R/2} V_b + \frac{R/2}{R+R/2} V_c$$

$$V_i = \frac{V_a}{3} + \frac{V_b}{3} + \frac{V_c}{3}$$

$$V_i = \frac{V_a + V_b + V_c}{3}$$

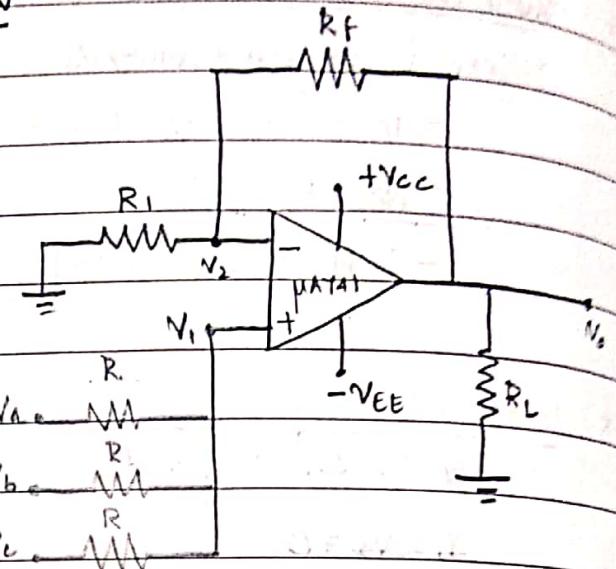

For noninverting configuration

$$V_o = \left[ 1 + \frac{R_f}{R_1} \right] V_i$$

$$\therefore V_o = \left[ 1 + \frac{R_f}{R_1} \right] \left[ \frac{V_a + V_b + V_c}{3} \right]$$

a. Summing Amplifier

If  $\left[ 1 + \frac{R_f}{R_1} \right]$  is number of inputs.

$$V_o = [V_a + V_b + V_c]$$

b. Averaging Amplifier

- No sign change or phase reversal occurs between the average of input and output.

- In non-inverting configuration  $V_i$  is the average of all the three inputs whereas in inverting configuration  $V_o$  is the average of all the three inputs.

$$V_o = - \left[ \frac{V_a + V_b + V_c}{3} \right]$$

## \* DIFFERENTIAL CONFIGURATION:

By using differential configuration we can construct summing amplifier and subtractor.


### a. Subtractor:

For inverting

$$V_o = -\frac{R_f}{R_i} V_i$$

$$\therefore V_o = -\frac{R}{R} [V_a - V_b]$$

$$V_o = V_b - V_a$$

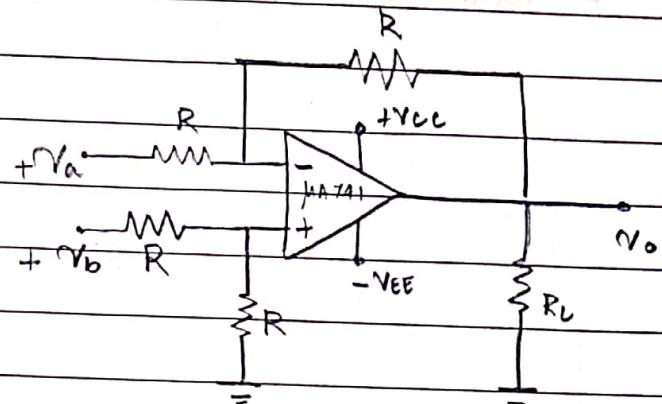

### b. Summing amplifier:


By superposition principle

$$V_{oa} = -\frac{R}{R} V_a = -V_a$$

$$V_{ob} = -\frac{R}{R} V_b = -V_b$$

$$V_{oc} = \left[ 1 + \frac{R}{R/2} \right] V_c = V_c$$
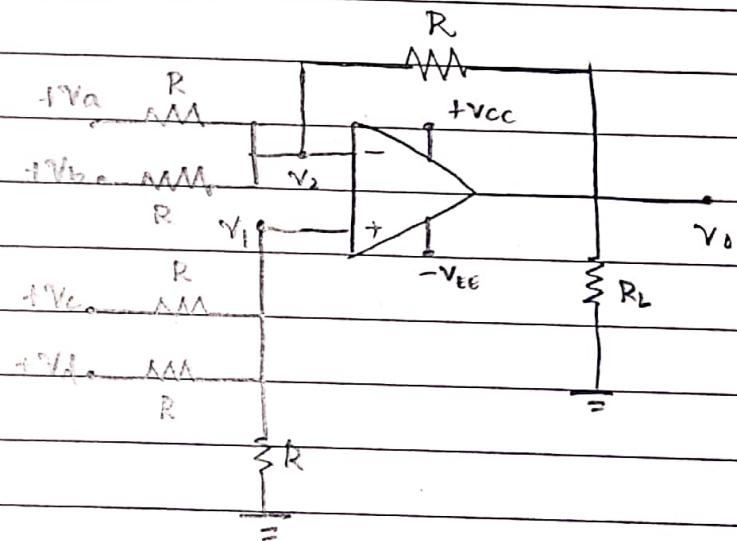
$$V_{od} = \left[ 1 + \frac{R}{R/2} \right] V_d = V_d$$



Output voltage

$$V_o = V_{oa} + V_{ob} + V_{oc} + V_{od}$$

$$V_o = -V_a - V_b + V_c + V_d$$

$$V_i = \frac{R/2}{R+R/2} V_c = \frac{V_c}{3}$$

$$V_i = \frac{R/2}{R+R/2} V_d = \frac{V_d}{3}$$

Q1: In the circuit shown in the figure (above)

$$R = 1k\Omega$$

$$V_a = 2V, V_b = 3V \text{ and } V_c = 4V, V_d = 5V$$

and the supply voltage is  $\pm 15V$ . Determine the output voltage  $V_o$ .


$$V_o = -2 - 3 + 4 + 5 = 4V$$

sol:

## \* Instrumentation Amplifier:


Application: used to measure physical quantities such as temperature, flow rate, pressure.
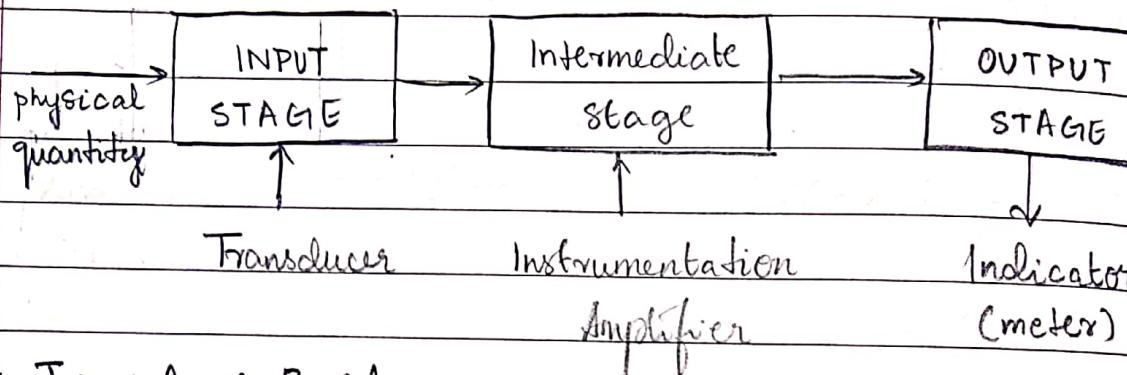
### - Basic Block Diagram of Instrumentation Amplifier


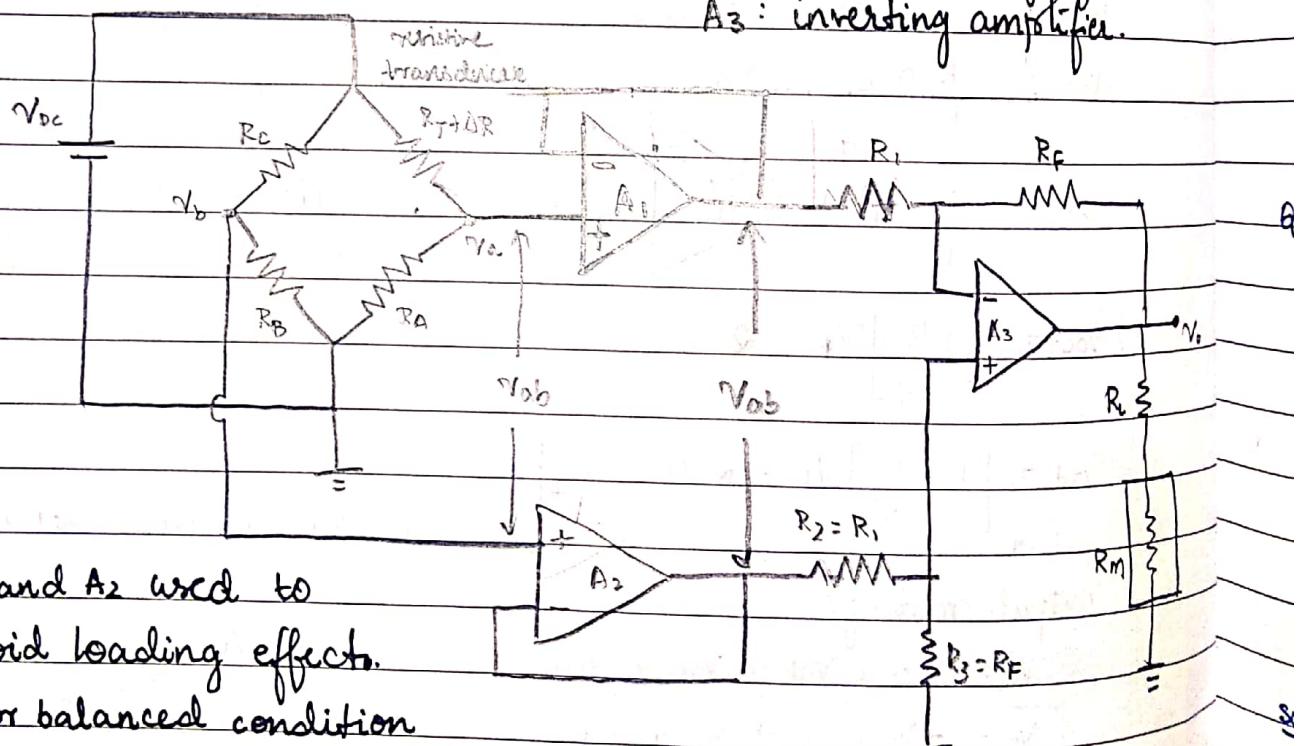
### - Transducer Bridge:

$A_1$  and  $A_2$ : voltage follower  
 $A_3$ : inverting amplifier.



$A_1$  and  $A_2$  used to avoid loading effects.

For balanced condition

$$V_a = V_b$$

$$R_a = R_b = R_c = R_T$$

$$\frac{R_c}{R_b} = \frac{R_T}{R_A}$$

$$V_{ab} = V_a - V_b$$

$$V_a = V_{DC} \left[ \frac{R_A}{R_A + (R_T + \Delta R)} \right]$$

$$V_b = V_{DC} \left[ \frac{R_B}{R_B + R_c} \right]$$

$$\therefore V_a - V_b = V_{DC} \left[ \frac{R_A}{R_A + (R_T + \Delta R)} - \frac{R_B}{R_B + R_c} \right]$$

Let  $R_A = R_B = R_C = R_T = R$

$$V_{ab} = V_{DC} \left[ \frac{R}{2R + \Delta R} - \frac{R}{2R} \right]$$

$$V_{ab} = V_{DC} \left[ \frac{2R - 2R - \Delta R}{2(2R + \Delta R)} \right]$$

$$V_{ab} = -V_{DC} \left[ \frac{\Delta R}{2(2R + \Delta R)} \right]$$

For A<sub>3</sub> amplifier

$$V_o = -\frac{R_f}{R_1} V_{ab}$$

$$V_o = -\frac{R_f}{R_1} \left[ -V_{DC} \left( \frac{\Delta R}{2(2R + \Delta R)} \right) \right] \quad 2R + \Delta R \approx 2R$$

$$\boxed{V_o = \frac{R_f}{R_1} V_{DC} \frac{\Delta R}{4R}} \Rightarrow V_o \propto \Delta R.$$

Q1: In an instrumentation amplifier  $R_1 = 1k\Omega$ ,  $R_f = 4.4k\Omega$ , then  $R_a = R_b = R_c = 100k\Omega$ , then  $V_{DC} = 5V$ . The opamp supply voltage is  $\pm 15V$ . The transducer is a thermistor with the following specifications:  $R_T = 100k\Omega$ . At the reference temperature of  $25^\circ C$ , the temperature coefficient of resistance is equal to  $1k\Omega/^\circ C$  or  $1\%/\text{ }^\circ C$ . Determine the output voltage at  $0^\circ C$  and at  $100^\circ C$ .

Sol: Given:  $R_1 = 1k\Omega$   $R_f = 4.4k\Omega$   $V_{DC} = 5V$

$R_a = R_b = R_c = 100k\Omega$   $+V_{CC} \& -V_{EE} = \pm 15V$

Reference temp:  $25^\circ C$ .  $R_T = 100k\Omega$

~~$\Delta R = 1k\Omega/^\circ C$~~

as  $R_a = R_b = R_c = R_T = 100k\Omega$  at  $25^\circ C$

It is balanced

hence  $V_a = V_b$  and  $V_o = 0$

Temp (0°C)

CASE 1:  $\Delta R = -1k \text{ (0-25)}$ 

$$\underline{\Delta R = 25k\Omega}$$

$$V_o = \frac{R_f}{R_i} V_{DC} \left[ \frac{\Delta R}{4R} \right]$$

$$V_o = \frac{4.7k}{1k} (5) \frac{25k}{4(100k)}$$

$$\underline{\underline{V_o = 1.468 \text{ V}}}$$

CASE 2:  $\Delta R = -1k (100-25)$ 

$$\underline{\Delta R = -75k\Omega}$$

$$V_o = \frac{R_f}{R_i} V_{DC} \left[ \frac{\Delta R}{4R} \right]$$

$$V_o = \frac{-4.7k}{1k} (5) \frac{75k}{4(100k)}$$

$$\underline{\underline{V_o = -4.4 \text{ V}}}$$

\* Voltage to Current Converter (Transconductance Amplifier)

Applications:

- low voltage ac or dc voltmeter
- zener diode tester
- LED

The conversion can be done by two methods

- a. V-I converter using floating load.
- b. V-I converter using grounded load.


2. V-I converter using floating load at 'a' due to virtual ground potential is  $V_i$

since  $I_B = 0$

$I_L$  is current across  $R_1$

$$\therefore V_i = I_L R_1 \quad \text{input}$$
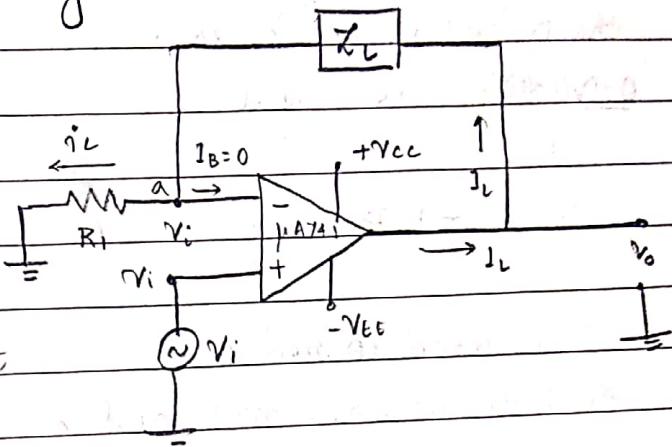
$$\therefore I_L = \frac{V_i}{R_1} \quad \text{output}$$



2. V-I converter using grounded load

Due to virtual ground at inverting terminal potential is  $V_i$ .

At node 'a'

$$I_L = i_1 + i_2$$

$$I_L = \frac{V_i - V_1}{R} + \frac{V_o - V_1}{R}$$


$$I_L = \frac{V_i - 2V_1 + V_o}{R}$$

$$I_L R = V_i - 2V_1 + V_o$$

$$V_1 = \frac{V_i + V_o - I_L R}{2} \quad \text{input}$$

$$\text{but } V_i = I_L R$$

$$I_L = \frac{V_i}{R}$$

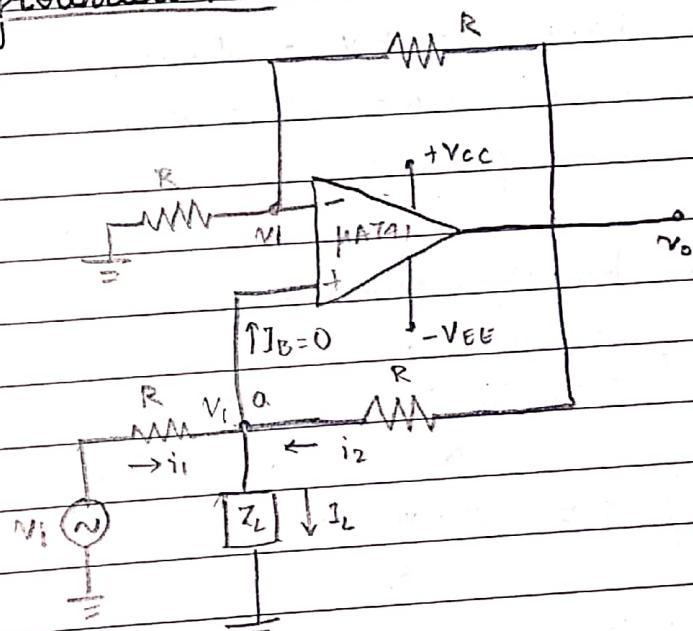

\* Current to Voltage converter (Transresistance Amplifier)  
Applications

- Photo diode


- Photo multiplier

- Photo FET Detector

Due to virtual ground  
the potential at 'a' is 0.

$$\frac{0 - V_o}{R_f} = I_s \text{ Input}$$

$$V_o = -I_s R_f \text{ output}$$

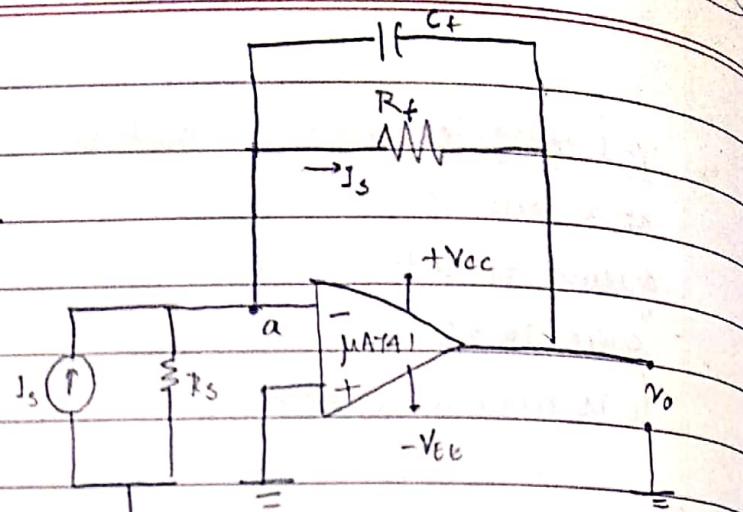


C\_F is used to reduce  
the high frequency noise and oscillations.

Q: For a voltage to current converter

shown,  $V_i = 5V$ ,  $R = 10k\Omega$ ,

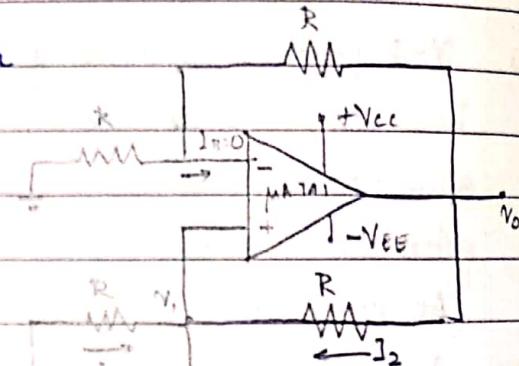$V_1 = 1V$ . Find the load current  
and output voltage.



Sol: Initially assume  $I_B = 0$

$$I_L = I_1 + I_2$$

$$I_L = \frac{V_i - V_1}{R} + \frac{V_o - V_1}{R}$$

$$I_L = \frac{V_i + V_o - 2V_1}{R}$$

$$I_L = \frac{5 + 2 - 2(1)}{10k}$$

$$I_L = 0.5mA$$

For non inverting amplifier

$$V_o = \left[ 1 + \frac{R_f}{R_1} \right] V_i$$

Here  $R_f = R_1 = R$

$$V_o = 2V_1$$

$$\underline{\underline{V_o = 2V}}$$

classmate

Date \_\_\_\_\_  
Page \_\_\_\_\_current Amplifier:

At output applying KVL

$$I_o = I_s + I_L$$

$$I_o = \frac{V_o}{R_1} + \frac{V_o}{R_L}$$

$$I_o = V_o \left[ \frac{1}{R_1} + \frac{1}{R_L} \right]$$


$$\therefore V_o = \frac{R_1 R_2}{R_1 + R_2} I_o$$

$$\text{but } V_o = I_L R_L$$

$$\frac{R_1 R_2}{R_1 + R_2} I_o = I_L R_L$$

$$\frac{R_1 R_2}{R_1 + R_2} [I_s + I_L] = I_L R_L$$

$$I_L = I_s \frac{R_1}{R_L}$$

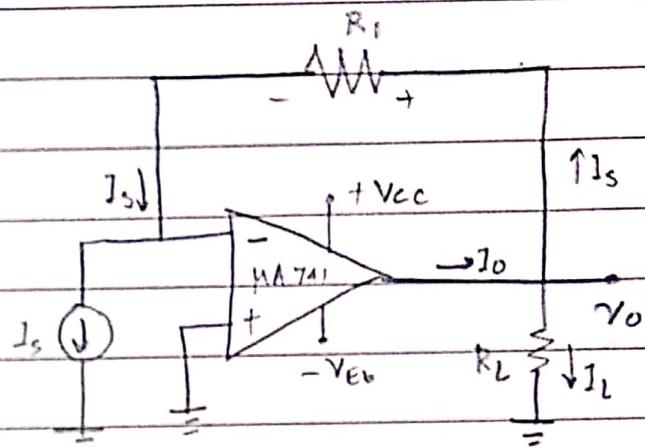

## Unit - 3

## LINEAR APPLICATIONS OF AN OP AMP - 11

Precision Rectifier:

The precision rectifier is obtained with an operational amplifier in order to have a circuit behave like an ideal diode and rectifier. It is useful for high precision signal processing.

Precision Half Wave Rectifier:

Due to virtual ground


$$V_A = V_B = 0$$

During positive half cycle

$D_1$  - forward biased

$D_2$  - reverse biased

$$\therefore V_o = 0$$

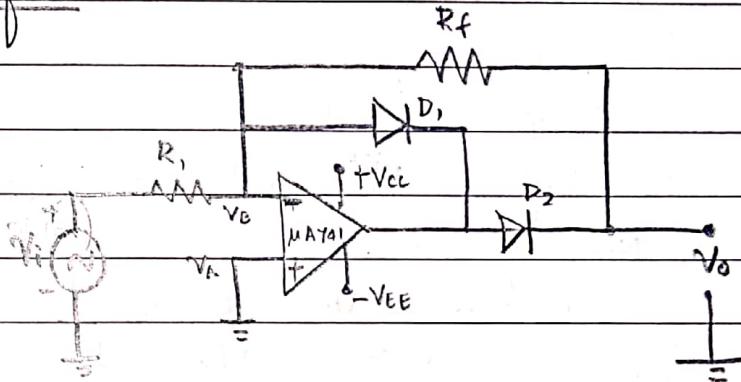

During negative half cycle

$D_1$  - reverse biased


$D_2$  - forward biased

Then it is like an inverting amplifier

$$\therefore V_o = -\frac{R_f}{R_1} V_i$$

$$\text{if } R_f = R_1, \text{ then } V_o = -V_i$$

(Positive)

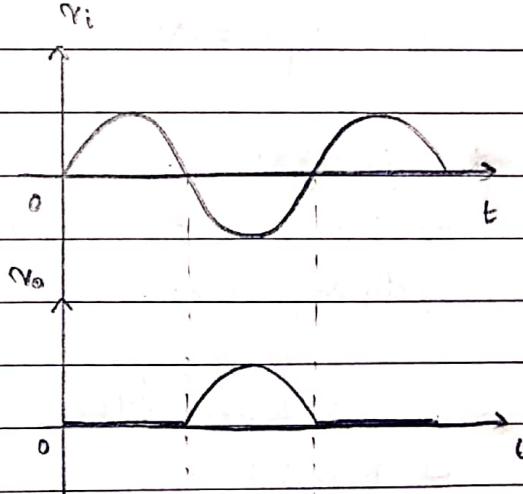Precision Full Wave Rectifier:

During positive half cycle


$A_1$  is negative

$\therefore D_1$  is forward biased

$D_2$  is reverse biased

Here op-amp 1 acts as inverting amplifier
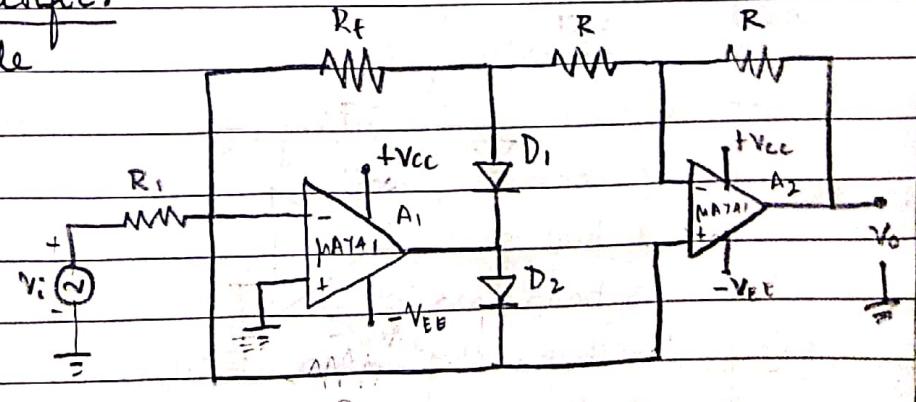
$$\therefore V_{o1} = -\frac{R_f}{R_1} V_{in} \Rightarrow V_{o1} = -V_{in}$$



If  $R_1 = R_f$  then  $V_o = -V_{in}$

Now op amp 2 acts as an inverting adder

$$\therefore V_o = - \left[ \frac{R}{R/2} V_{o1} + \frac{R}{R} V_{in} \right]$$

$$\text{but } V_{o1} = -V_{in}$$

$$\therefore V_o = -[-2V_{in} + V_{in}]$$

$$\boxed{V_o = V_{in}}$$

During negative half cycle  
 $A_1$  is positive


$\therefore D_1$  is reverse biased and  $D_2$  is forward biased

But due to virtual ground output of opamp 1,  $V_{o1} = 0$ .

Now opamp 2 has an output

$$V_o = - \left[ \frac{R}{R} V_{in} + \frac{R}{R/2} V_{o1} \right]$$

$$\therefore \boxed{V_o = -V_{in}}$$

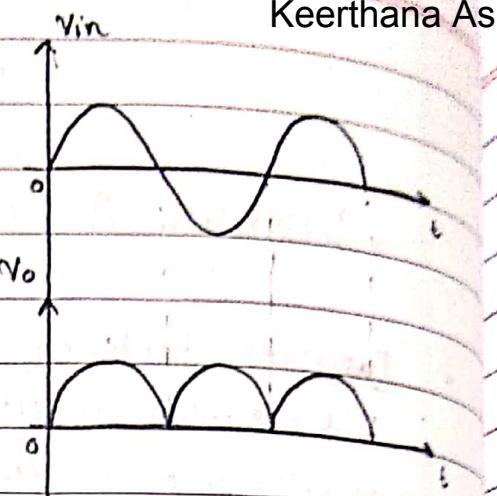

### \* Filters:

- Based on the nature of signal processing, filters are classified as:

a. Analog filter

b. Digital filter.

- Based on the components used, filters are classified as:

a. Active filters

b. Passive filters.

- Based on the frequency, filters are classified as:

a. lowpass filter.

b. high pass filter.

3. bandpass filter.

4. band stop / band elimination / band reject filter.

5. All pass filter.


\* Active filters:

Passive filters ( $R, L, C$ ) along with op-amp / transistor forms an active filter.

1. Low pass filter:

It allows the frequency range upto the cut off frequency  $f_H$ , beyond which it attenuates.


Frequency response

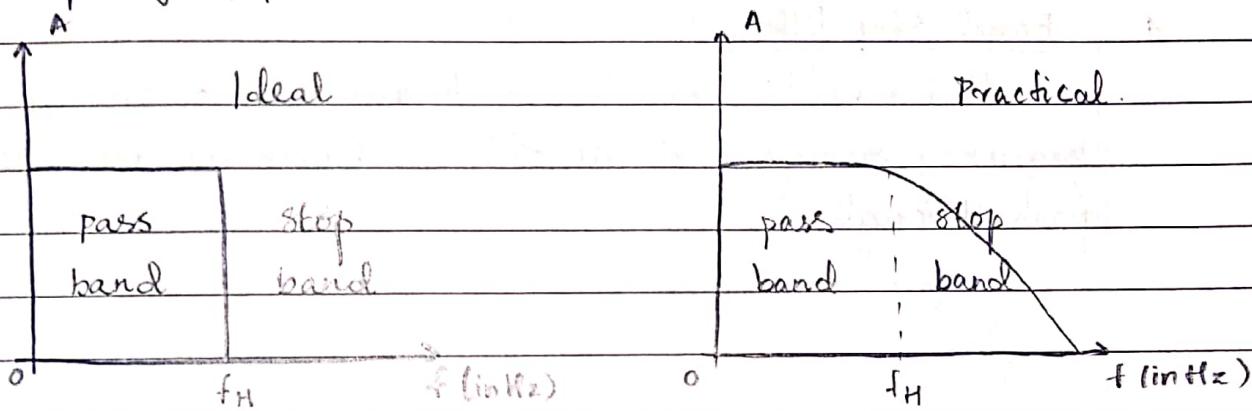

2. High pass filter:

It allows the frequency range beyond the cut off frequency,  $f_L$ , until  $f_H$  it is attenuated.

Frequency response

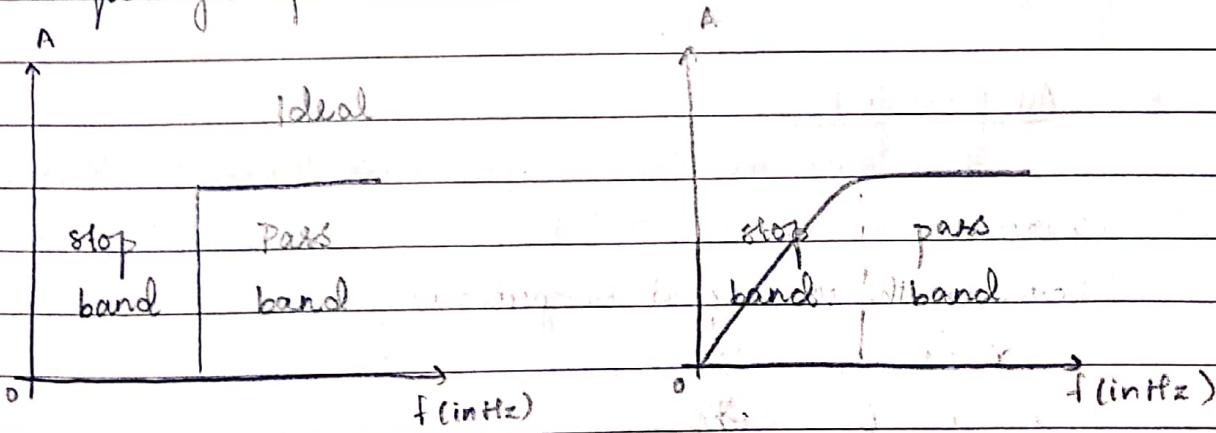


3. Band Pass filter:

It allows the band of frequency of the range  $f_L$  to  $f_H$ . Other frequencies are attenuated.


(combination of high pass and low pass filter)

## Frequency response

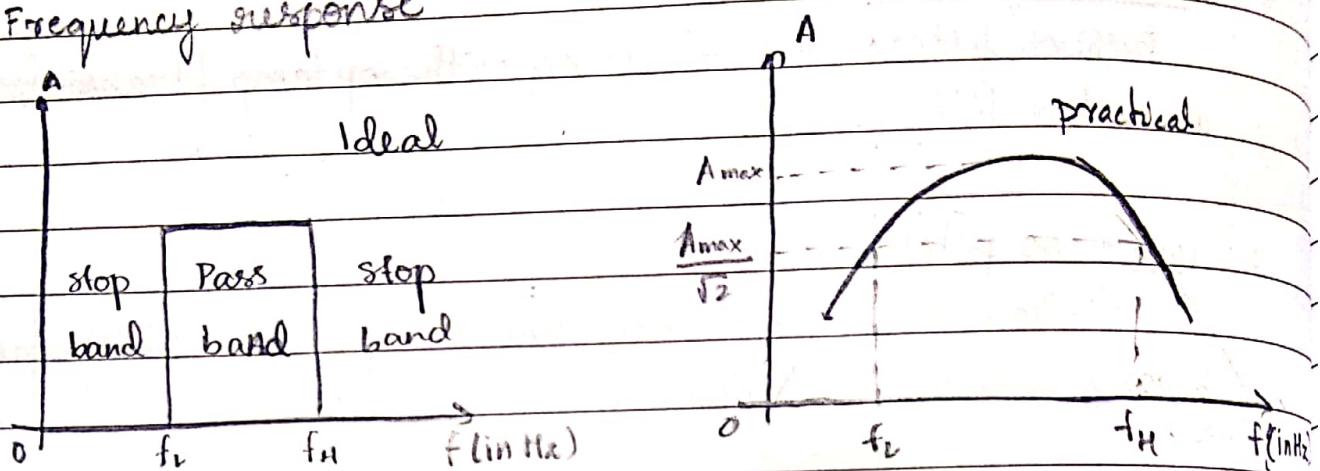


4. Band Stop filter (notch filter: based on shape of frequency response)  
It blocks / attenuates the frequencies from  $f_L$  to  $f_H$  frequency range and all other frequencies are allowed to pass through.

## Frequency response

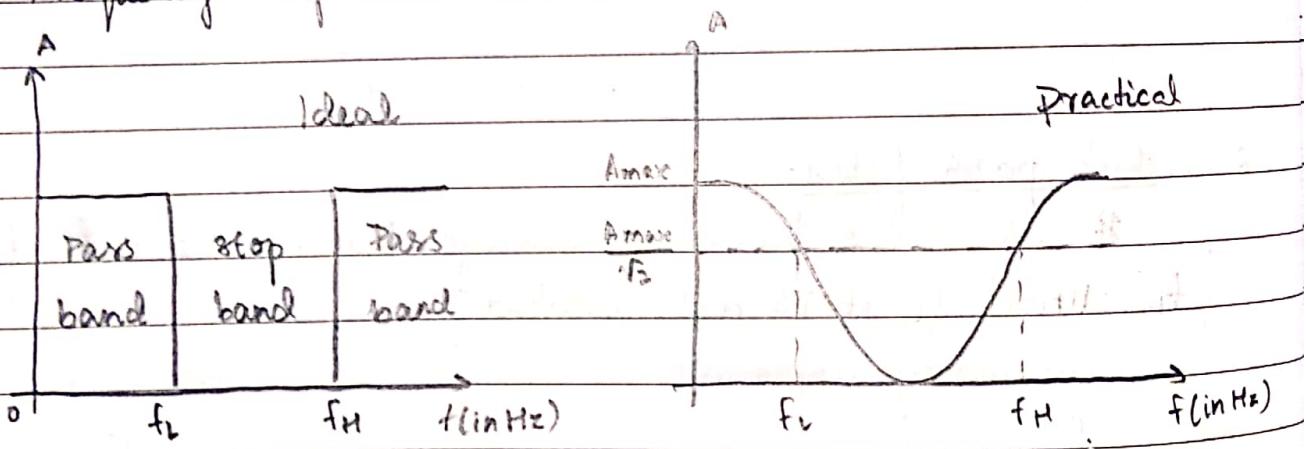

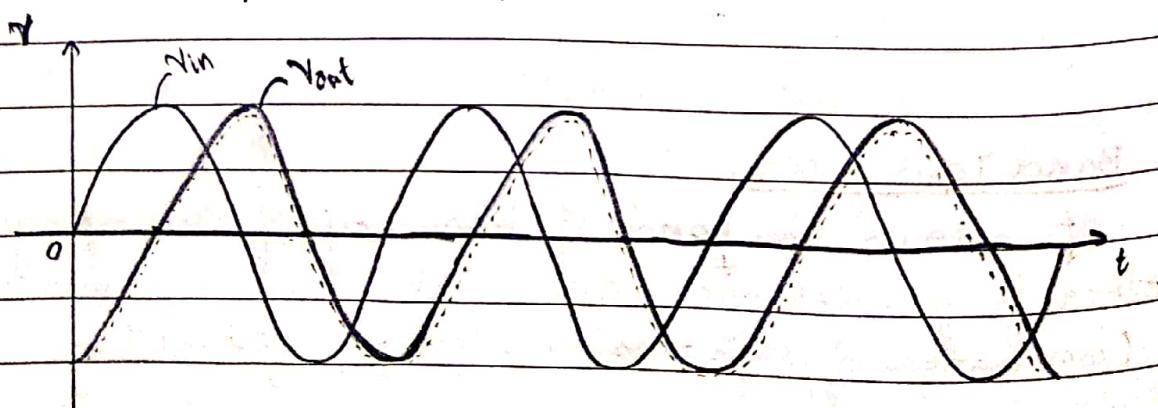5. All pass filter

It allows all frequency to pass through, that is from zero to maximum. But there is around  $90^\circ$  phase shift between the input and output.



\* Order of filter:

Depending upon the gain roll off the filters may be classified as first order, second order, third order, etc.

Order of filter	Rate of roll off of the gain
I order	-20 dB/decade
II order	-40 dB/decade
III order	-60 dB/decade
IV order	-80 dB/decade

Note: Number of RC network is equal to the order of the filter.

\* Filters are also classified as:


1. Butterworth filter
2. Chebyshev filter
3. Elliptic filter
4. Bessel filter

\* 1 order Low Pass Butterworth filter:

For a non-inverting amplifier

$$A = 1 + \frac{R_f}{R_1}$$
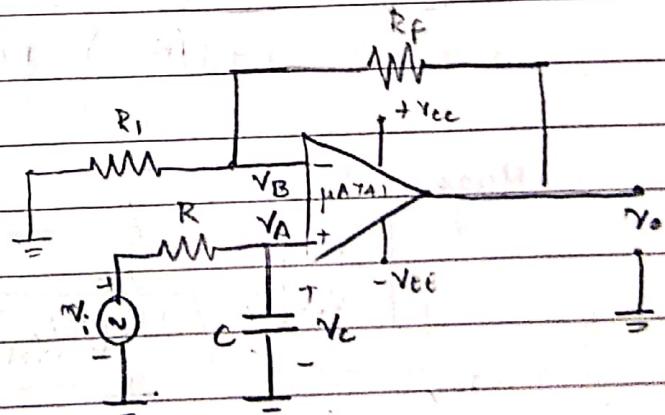
$$\therefore V_o = \left[ 1 + \frac{R_f}{R_1} \right] V_A \quad \textcircled{1}$$



By superposition.

$$V_A = V_c = -j \times C \cdot V_i$$

$$R - j \times C$$

$$V_A = V_c = \frac{-j}{2\pi f C} V_i = \frac{-j V_i}{2\pi f C R - j}$$

$$V_A = V_C = \frac{-jV_i}{2\pi f R C - j}$$

$$V_A = V_C = \frac{V_i / j}{2\pi f R C + j}$$

$$\frac{2\pi f R C + j}{j}$$

$$V_A = V_C = \frac{V_i / j}{j^2 2\pi f R C + 1}$$

$$\therefore V_A = V_C = \frac{V_i}{j^2 2\pi f R C + 1}$$

Substituting in eq ①

$$V_o = \left[ 1 + \frac{R_f}{R_1} \right] \left[ \frac{V_i}{1 + j^2 2\pi f R C} \right]$$

$$\text{Here } A_f = 1 + \frac{R_f}{R_1} \text{ and } \frac{1}{j^2 2\pi f R C} = f_H$$

$$\therefore V_o = A_f \left[ \frac{V_i}{1 + j f / f_H} \right]$$

$$\boxed{\frac{V_o}{V_i} = \frac{A_f}{1 + j \left( \frac{f}{f_H} \right)}}$$

Magnitude

$$\boxed{\left| \frac{V_o}{V_i} \right| = \frac{A_f}{\sqrt{1 + \left( \frac{f}{f_H} \right)^2}}}$$

Phase angle

$$\boxed{\phi = \tan^{-1} \left( \frac{f}{f_H} \right)}$$

Frequency response of Low pass Butterworth filter:

$$\frac{V_o}{V_i} = \frac{A_f}{1 + j(f/f_H)}$$

CASE 1: For frequency:  $f = 0$ .


$$A = A_f$$

CASE 2: For frequencies  $f < f_H$

$$A = A_f$$

CASE 3: For frequency  $f = f_H$

$$A = \frac{A_f}{\sqrt{2}} = 0.707 A_f$$

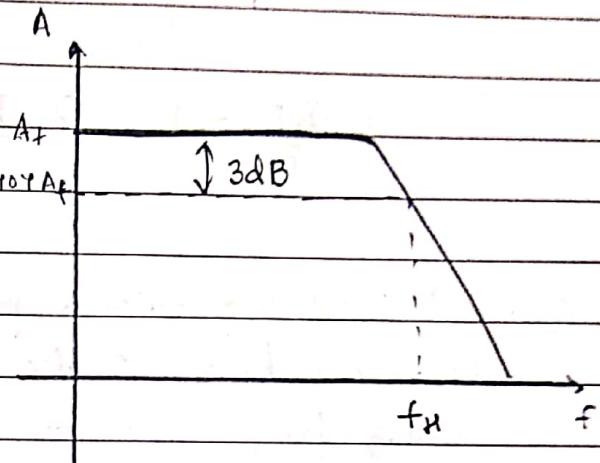

CASE 4: For frequencies  $f > f_H$

$$A < A_f$$

Design rule for low pass Butterworth filter:

Assume  $C \leq 1\mu F$ .

$$f_H = \frac{1}{2\pi RC}$$

$$\text{Gain: } A_f = 1 + \frac{R_f}{R_1}$$

Frequency scaling technique to find new resistance

$$\text{Ex: } f_H = 10 \text{ kHz} \quad f_H' = 12 \text{ kHz}$$

$$R_{\text{new}} = R \left( \frac{f_H}{f_H'} \right)$$

Q: Design a low pass filter at a cut off frequency of 10 kHz with a pass band gain of 2.

Sol:

$$\text{Given: } f_H = 10 \text{ kHz} \quad A_f = 2$$

$$\text{Assuming } C = 0.01 \mu F$$

$$f_H = \frac{1}{2\pi RC} \Rightarrow R = \frac{1}{2\pi(10k)(0.01\mu)} = \underline{\underline{1.59 k\Omega}}$$

$$A_f = 1 + \frac{R_f}{R_1}$$

$$\omega = 1 + \frac{R_f}{R_1}$$

$$\frac{R_f}{R_1} = 1 \Rightarrow R_f = R_1 \quad \text{For } R_f = 10k\Omega$$

$$R_1 = 10k\Omega$$

Q2: If in the previous problem the cut off frequency is changed from 10 kHz to 12 kHz, find the new value of R using frequency scaling technique.

Sol: Given:  $f_H = 10 \text{ kHz}$   $f_{H'} = 12 \text{ kHz}$

$$R_{\text{New}} = R \left( \frac{f_H}{f_{H'}} \right)$$

$$R_{\text{New}} = 1.59k \left( \frac{10k}{12k} \right)$$

$$R_{\text{New}} = 1.326k\Omega$$

### \* II Order Low Pass Butterworth Filter:

Let  $R_2 = R_3 = R$


and  $C_2 = C_3 = C$

$$f_H = \frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}}$$

$$\therefore f_H = \frac{1}{2\pi R C}$$

Magnitude

$$\left| \frac{V_o}{V_i} \right| = \frac{A_f}{\sqrt{1 + \left( \frac{f}{f_H} \right)^4}}$$

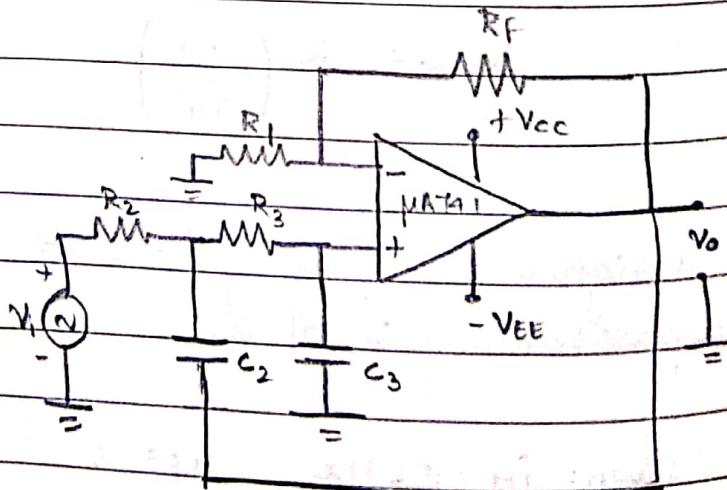

Designing of 11 order Butterworth low pass filter:

Assume  $C < 1\mu F$

$$A_f = 1 + \frac{R_f}{R_1}$$

$$f_H = \frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}}$$

If  $R_2 = R_3$  &  $C_2 = C_3$  - then  $f_H = \frac{1}{2\pi R C}$

$$R_1 \leq 100 k\Omega$$

If the gain value is not given then assume that

$$A_f = 1 + \frac{R_f}{R_1} = 1.586$$

$$\text{where } \frac{R_f}{R_1} = 0.586 \Rightarrow R_f = 0.586 R_1$$

- Q1: Design a 11 order low pass Butterworth filter to have a higher cut-off frequency of 1.5 kHz.

Sol: Given:  $f_H = 1.5 \text{ kHz}$

Assuming  $C = 0.05 \mu F$

$$f_H = \frac{1}{2\pi R C}$$

$$\Rightarrow R = \frac{1}{2\pi f_H C} = \frac{1}{2\pi (1.5 \text{ k})(0.05 \mu)} = \underline{\underline{2.12 k\Omega}}$$

since  $A_f$  is not given, assuming  $A_f = 1.586$

$$\therefore 1 + \frac{R_f}{R_1} = 1.586$$

$$\frac{R_f}{R_1} = 0.586$$

$$R_f = 0.586 R_1$$

Assuming  $R_1 = 2.12 k\Omega$

$$\underline{\underline{R_f = 15.822 k\Omega}}$$

★

1 Order high pass Butterworth Filter:

for non-inverting amplifier

$$A = 1 + \frac{R_f}{R_1}$$

$$\therefore V_o = \left[ 1 + \frac{R_f}{R_1} \right] V_A \quad \text{--- (1)}$$

By superposition

$$V_A = \frac{RV_i}{R - jX_C}$$

$$V_A = \frac{RV_i}{jX_C \left( \frac{R}{jX_C} - 1 \right)} \quad \text{where } X_C = \frac{1}{2\pi f C}$$

$$V_A = \frac{R V_i}{\frac{j}{2\pi f C} \left[ \frac{2\pi f R C}{j} - 1 \right]} = \frac{R V_i}{\frac{j}{2\pi f C} \left[ \frac{2\pi f R C - j}{j} \right]}$$

$$V_A = \frac{\frac{2\pi f R C V_i}{2\pi f R C - j}}{2\pi f R C + j} = \frac{2\pi f R C V_i}{2\pi f R C + j}$$

$$V_A = \frac{j 2\pi f R C V_i}{j 2\pi f R C + j}$$

Substituting in eq (1)

$$V_o = \left[ 1 + \frac{R_f}{R_1} \right] \left[ \frac{j 2\pi f R C V_i}{j 2\pi f R C + j} \right]$$

$$V_o = \left[ 1 + \frac{R_f}{R_1} \right] \left[ \frac{j f / f_L}{j f / f_L + 1} \right] V_i$$


$$\frac{1}{2\pi R C} = f_L$$

$$\text{Here, } \left[ 1 + \frac{R_f}{R_1} \right] = A_f$$

$\frac{V_o}{V_i} = \frac{A_f j (f / f_L)}{j (f / f_L) + 1}$
---

Magnitude

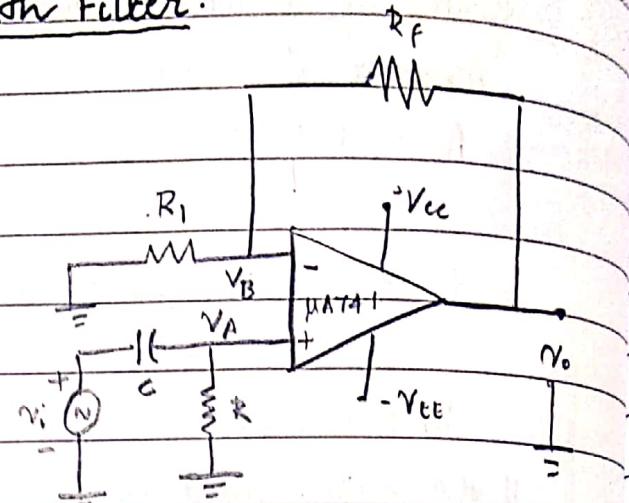$\left  \frac{V_o}{V_i} \right  = \frac{A_f (f / f_L)}{\sqrt{1 + (f / f_L)^2}}$
---



Frequency response of High Pass Butterworth filter:

$$\frac{V_o}{V_i} = \frac{A_f}{1 + j(f/f_L)}$$

$$\frac{V_o}{V_i} = \frac{1}{1 + j(f/f_L)}$$

CASE 1:  $f = 0$


$$A = A_f$$

CASE 2:  $f < f_L$

$$A < A_f$$

CASE 3:  $f = f_L$

$$A = \frac{A_f}{\sqrt{2}} = 0.707 A_f$$

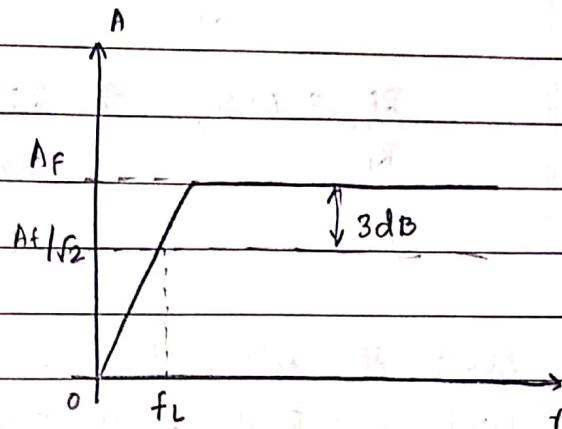

CASE 4:  $f > f_L$

$$A = A_f$$

\* 11 Order High Pass Butterworth Filter:


Let  $R_2 = R_3 = R$  and  $C_2 = C_3 = C$

$$f_L = \frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}}$$

$$\therefore f_L = \frac{1}{2\pi R C}$$

Magnitude

$$\left| \frac{V_o}{V_i} \right| = \frac{A_f (f/f_L)}{\sqrt{1 + \left( \frac{f}{f_L} \right)^4}}$$

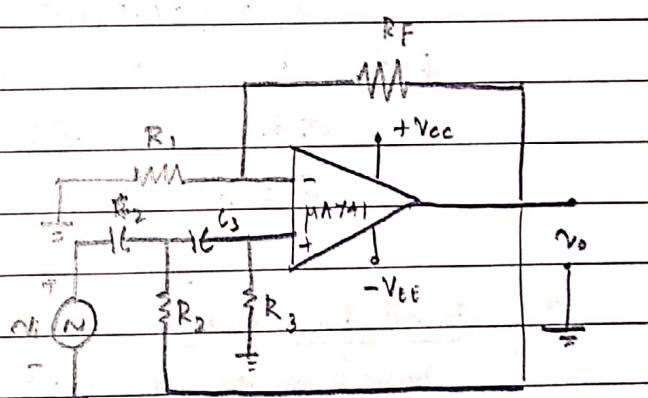

Q1: Design a first order high pass filter to have a lower cut-off frequency of 1.5 kHz and the pass band gain of 1.5.

Sol: Given:  $f_L = 1.5 \text{ kHz}$   $A = 1.5$

Assuming  $C = 0.01 \mu\text{F}$

$$f_L = \frac{1}{2\pi R C} \Rightarrow R = \frac{1}{2\pi f L} = \frac{1}{2\pi (1.5k)(0.01\mu)} = 10.61 \text{ k}\Omega$$

$$A_f = 1 + \frac{R_f}{R_1}$$

$$1.5 = 1 + \frac{R_f}{R_1}$$

$$\frac{R_f}{R_1} = 0.5 \Rightarrow R_f = 0.5 R_1$$

Assuming  $R_1 = 10k\Omega$

$$\therefore \underline{R_f = 5k\Omega}$$

Q2: Obtain the value of lower cut off frequency of 11 order high pass Butterworth filter. Given:  $R_1 = 4.9k\Omega$  and  $R_2 = R_3 = 10k\Omega$   
 $C_2 = C_3 = 0.01\mu F$ .

Sol: Given:  $R_1 = 4.9k\Omega$

$$R_2 = R_3 = 10k\Omega$$

$$C_2 = C_3 = 0.01\mu F$$

$$f = \frac{1}{2\pi R C} = \frac{1}{2\pi (10k)(0.01\mu)}$$

$$\underline{f = 1.59 \text{ kHz}}$$

### \* Band Pass Filter:

Based on the Q factor it is classified as

1. Wide band pass filter
2. Narrow band pass filter

$$Q\text{-factor} = \frac{f_c}{BW} \Rightarrow Q \propto \frac{1}{BW} \quad Q = \frac{f_c}{f_H - f_L}$$



If  $Q < 10$ : wide band pass filter

If  $Q > 10$ : narrow band pass filter.

Band pass filter allows all the frequencies in the range from lower cut off frequency  $f_L$  to higher cut off frequency  $f_H$ . All other frequencies are attenuated.

- Wide Bandpass Filter: (high pass filter + low pass filter)

Frequency response

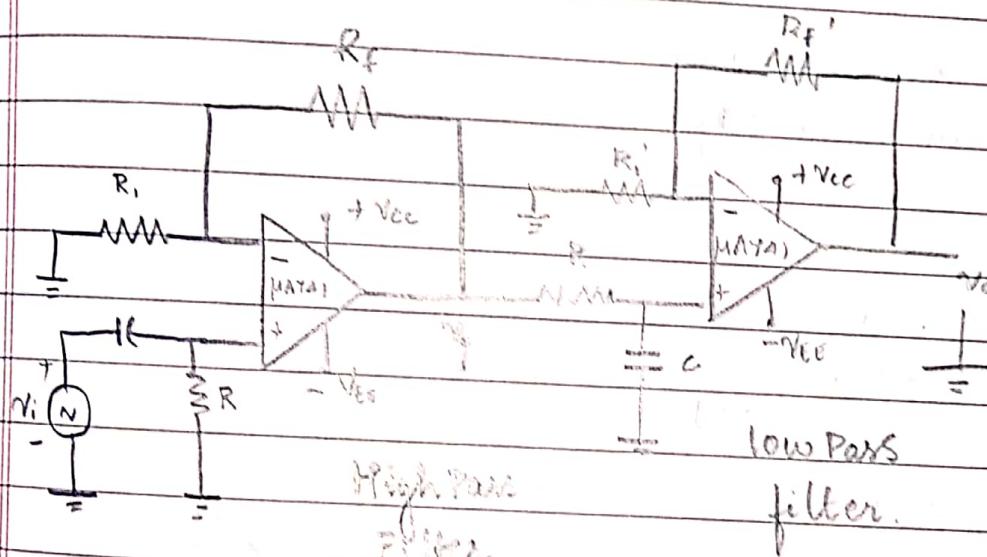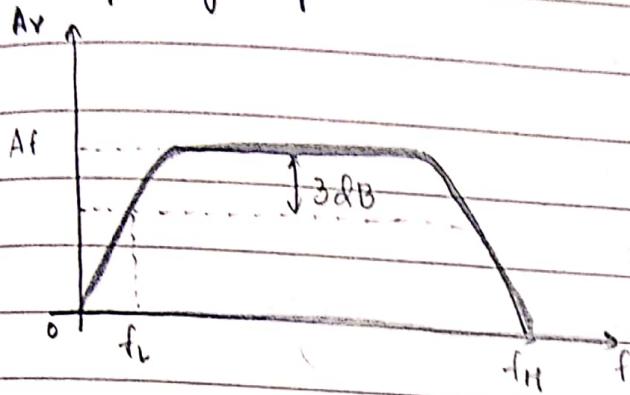

Gain is given by

$$A_f = A_1 \cdot A_2$$

$$\text{High pass filter: } A_1 = A_{f_1} \left( \frac{f}{f_L} \right)$$

$$\sqrt{1 + \left( \frac{f}{f_L} \right)^2}$$

$$\text{Low pass filter: } A_2 = \frac{A_{f_2}}{\sqrt{1 + \left( \frac{f}{f_H} \right)^2}}$$

$$\therefore A_f = \frac{A_{f_1} \left( \frac{f}{f_L} \right)}{\sqrt{1 + \left( \frac{f}{f_L} \right)^2}} \cdot \frac{A_{f_2}}{\sqrt{1 + \left( \frac{f}{f_H} \right)^2}}$$

Q1:

Design a wide band pass filter to have lower and higher cut off frequency of 500Hz and 1.5 kHz respectively and a pass band gain of 4. Also calculate Q-factor of the filter.

Sol:

$$\text{Given: } f_L = 500 \text{ Hz} \quad f_H = 1.5 \text{ kHz}$$

$$A_f = 4$$

To design high pass filter  
assuming  $C_1 = 0.01 \mu\text{F}$ .

$$f_L = \frac{1}{2\pi RC}$$

$$\Rightarrow R = \frac{1}{2\pi f_L C_1} = \frac{1}{2\pi (500)(0.01\mu)} = 31.8 \text{ k}\Omega$$

To design low pass filter

assuming  $C_2 = 0.03 \mu\text{F}$ .

$$f_H = \frac{1}{2\pi R_2 C_2}$$

$$\Rightarrow R = \frac{1}{2\pi f_H C_2} = \frac{1}{2\pi (1.5k)(0.03\mu)} = 10.61 \text{ k}\Omega$$

$$A_f = 4$$

$$A_1 = A_2 = \sqrt{4} = 2 \quad (\because A_1 A_2 = 4)$$

$$Q = 1 + \frac{R_F}{R_1}$$

$$\therefore R_F = R_1 = 10 \text{ k}\Omega$$


$$Q - \text{factor} = \frac{f_C}{f_H - f_L}$$


$$Q = \frac{\sqrt{f_L f_H}}{f_H - f_L}$$

$$Q = \frac{\sqrt{500(1.5k)}}{1500 - 500} = 0.866$$

### \* Narrow Band Pass Filter:

Frequency response

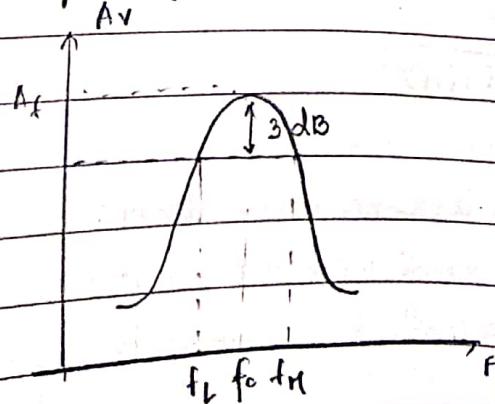

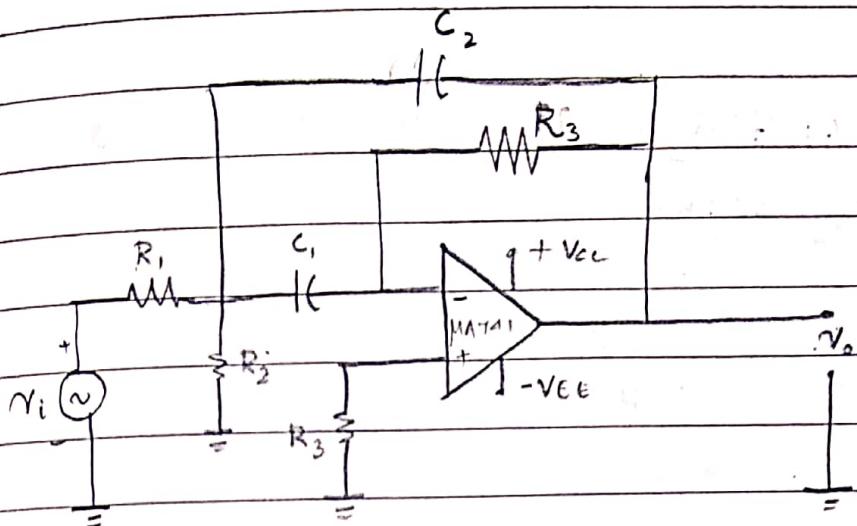

Design rule:

Take  $C_1 = C_2 = C$  and  $C < 1 \mu\text{F}$

calculate all resistors based on the relationship given below:

$$R_1 = \frac{Q}{2\pi f_c C A_f}$$

$$A_f = \frac{R_3}{2R_1}$$

$$R_2 = \frac{Q}{2\pi f_c C (2Q^2 - A_f)}$$

$$A_f < 2Q^2$$

$$R_3 = \frac{Q}{\pi f_c C}$$

If the center frequency changes from  $f_c$  to  $f_c'$

$$R_2' = R_2 \left( \frac{f_c}{f_c'} \right)^2$$

Q1: Design a narrow pass band filter for which  $f_c = 1\text{kHz}$ ,  $Q = 3$  and  $A_f = 10$ . How do you change the centre frequency to  $1.2\text{kHz}$  keeping  $A_f$  and BW constant.

Sol:

Given:  $f_c = 1\text{kHz}$ ;  $Q = 3$ ;  $A_f = 10$ .

$$f_c' = 1.2\text{kHz}$$

$$C_1 = C_2 = C = 0.01\mu\text{F}$$

$$R_1 = \frac{Q}{2\pi f_c C A_f} = \frac{3}{2\pi (1\text{k})(0.01\mu\text{F})(10)}$$

$$R_1 = 4.47\text{k}\Omega$$

$$R_2 = \frac{Q}{2\pi f_c C (2Q^2 - A_f)} = \frac{3}{2\pi (1k)(0.01\mu)(2(9)-10)}$$

$$\underline{R_2 = 5.9k\Omega}$$

$$R_3 = \frac{Q}{\pi f_c C} = \frac{3}{\pi (1k)(0.01\mu)}$$

$$\underline{R_3 = 95.49k\Omega}$$

$$R'_2 = R_2 \left( \frac{f}{f'} \right)^2 = 5.9k \left[ \frac{1k}{1.2k} \right]^2$$

$$\underline{R'_2 = 4.14k\Omega}$$

\* Band stop Filter:

It is classified as:


1. Wide band stop filter
2. Narrow band stop filter.


- Wide band stop filter:

(Circuit filter + high pass filter + running amplifier)

- The lowpass and the high pass filter has equal pass band gain. Frequency response  
This condition has to be satisfied for a wide band stop filter.

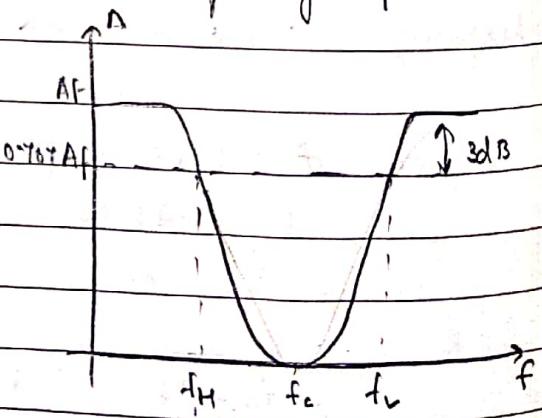- The lower cut off frequency  $f_L$  of high pass filter should be greater than higher cut off frequency  $f_H$  of low pass filter.



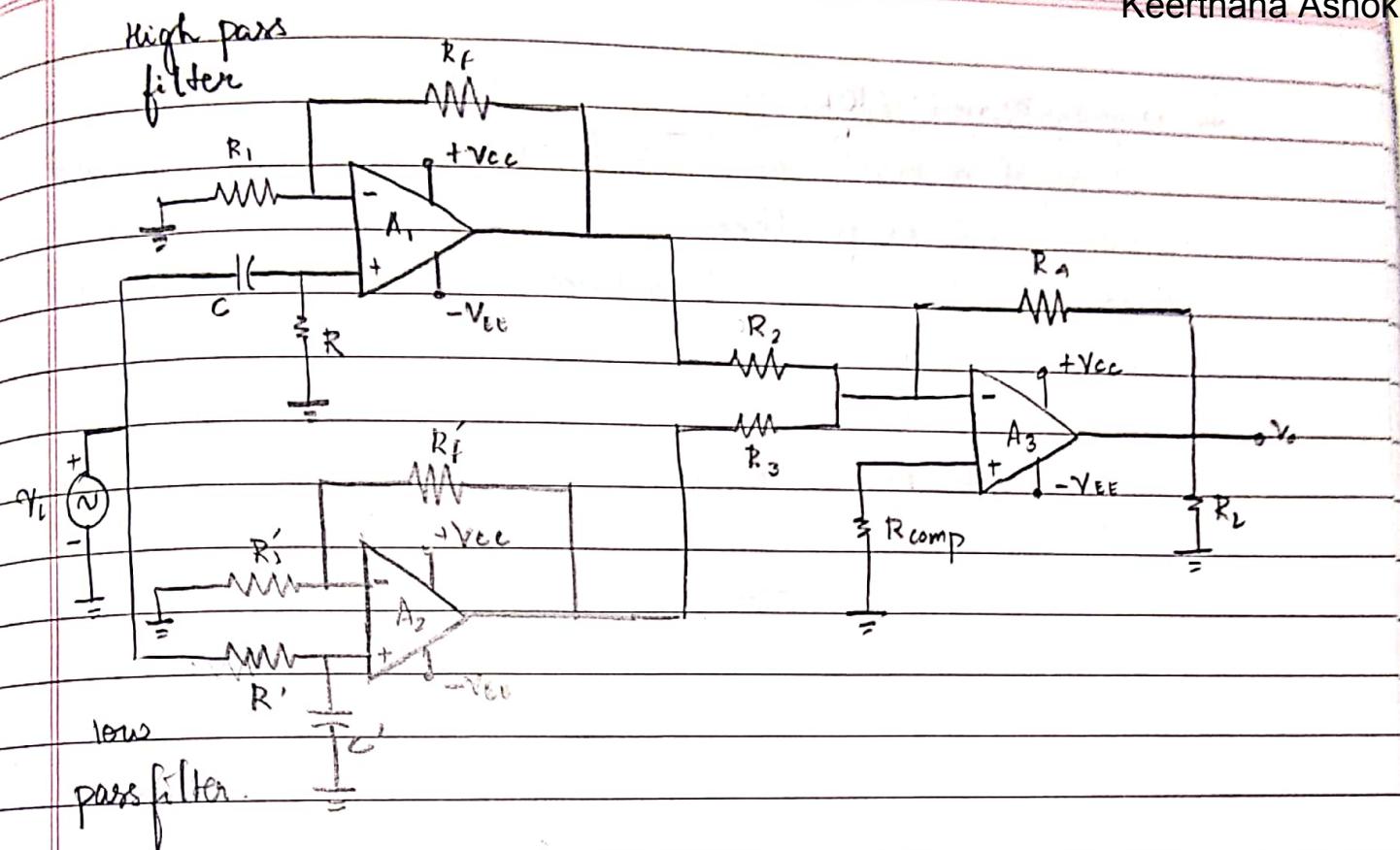

Q: Design a wide band stop filter to have  $f_L = 500\text{Hz}$  and  $f_U = 1.5\text{kHz}$ .

Sol: Given:  $f_L = 1.3\text{kHz}$ ;  $f_H = 500\text{Hz}$

Assuming  $C = 0.05\mu\text{F}$  and  $C' = 0.01\mu\text{F}$

$$t_H = \frac{1}{2\pi f_H C}$$

$$\Rightarrow R = \frac{1}{2\pi f_H C} = \frac{1}{2\pi(500)(0.05\mu)} = 6.36\text{k}\Omega$$

$$t_L = \frac{1}{2\pi R'C'}$$

$$\Rightarrow R' = \frac{1}{2\pi f_L C'} = \frac{1}{2\pi(1.5k)(0.01\mu)} = 10.61\text{k}\Omega$$

$$R'_f = R_f = 10\text{k}\Omega$$


$$R_1 = R_F = 10\text{k}\Omega$$

If the gain of the summing amplifier is assumed as 1.  
 $R_2 = R_3 = R_4 = 10\text{k}\Omega \Rightarrow R_{comp} = \frac{10k}{3} = 3.33\text{k}\Omega$


Narrow Band stop Filter: (Notch filter)

To reject a signal at a particular frequency we use narrow band stop filter.

It is used in a twin-T network

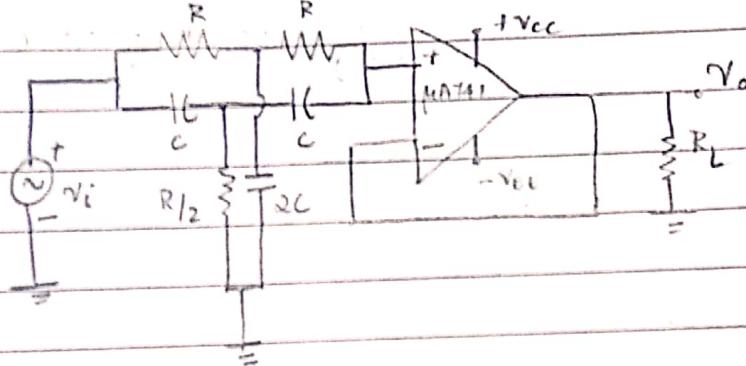

Frequency response

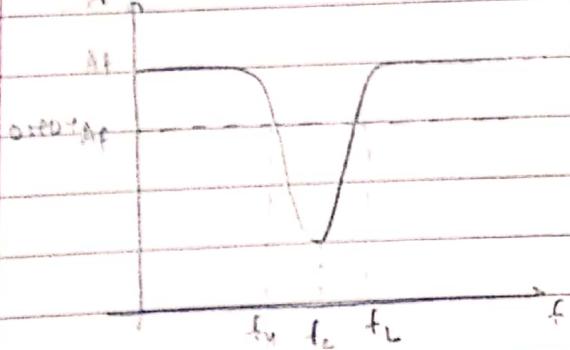

$$\text{Notch filter frequency} \quad f_N = \frac{1}{2\pi RC}$$

Q: Design an active notch filter to eliminate 100Hz frequency

Sol:  $f_N = 100 \text{ Hz}$

Assuming  $C = 0.01 \mu\text{F}$

$$f_N = \frac{1}{2\pi RC}$$

$$\rightarrow R = \frac{1}{2\pi f_N C} = \frac{1}{2\pi(100)(0.01\mu)} = 159.1 \text{ k}\Omega$$

$$\underline{R/2 = 79.5 \text{ k}\Omega} \quad \underline{\omega C = 0.02 \text{ MF}}$$

All Pass Filter:

It allows all the frequencies with certain phase shift.

Let us consider  $R_1 = R_f$

Using superposition

$R_1$  is grounded hence acts as non inverting amplifier.

$$\therefore V_{o1} = \left[ 1 + \frac{R_f}{R_1} \right] V_A$$

$$V_{o1} = 2 V_A \quad (\because R_f = R_1)$$

$R_f$  is grounded hence acts as inverting amplifier.

$$V_{o2} = -\frac{R_f}{R_1} V_B$$

$$V_{o2} = -V_B \quad (\because R_f = R_1)$$

By Voltage divider rule

$$V_A = \left[ \frac{-jX_C}{R - jX_C} \right] V_i$$

$$\text{but } X_C = \frac{1}{2\pi f C}$$

$$V_A = \frac{V_i}{1 + j 2\pi f R C}$$

Therefore


$$V_o = V_{o1} + V_{o2}$$

$$V_o = 2 V_A - V_i$$

~~Therefore~~

$$V_o = \frac{2 V_i}{1 + j 2\pi f R C} - V_i$$
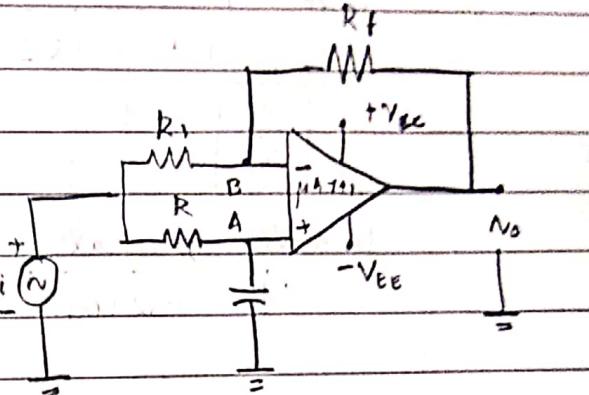
$$V_o = V_i \left[ \frac{2}{1 + j 2\pi f R C} - 1 \right]$$



$$V_o = V_i \left[ \frac{1 - j2\pi f R C}{1 + j2\pi f R C} \right]$$

$$\left| \frac{V_o}{V_i} \right| = \sqrt{1 + (2\pi f R C)^2}$$

$$\left| \frac{V_o}{V_i} \right| = 1$$

In order to analyse phase shift  $\phi$ , we have:

$$\phi = -2 \tan^{-1}(2\pi f R C)$$

If the phase shift is negative, then the output lags behind the input by an angle  $\phi$ .

If the phase shift is positive, then the output leads the input by an angle  $\phi$ .

Q: Find the phase shift in an all pass filter given a signal frequency  $2k\text{Hz}$  and  $R = 20\text{k}\Omega$  and  $C = 0.01\mu\text{F}$ .

Sol: Given:  $f = 2k\text{Hz}$

$$R = 20\text{k}\Omega$$

$$C = 0.01\mu\text{F}$$

$$\phi = -2 \tan^{-1}(2\pi f R C)$$

$$\phi = -2 \tan^{-1}(2\pi(2k)(20k)(0.01\mu))$$


$$\phi = -2 \tan^{-1}(2.5132)$$

$$\phi = \underline{-136.6^\circ}$$

Data Converters:Digital to Analog Data Converters:

It can be done by:

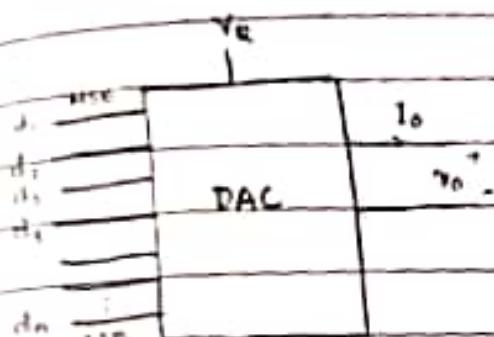1. Binary Weighted Resistor
2. R-R Ladder Network.




Output voltage

$$V_0 = k V_{FS} (d_3 \cdot 2^3 + d_2 \cdot 2^2 + \dots + d_0 \cdot 2^0)$$

where  $k$ : scaling factor = 3

$V_{FS}$ : Full scale output voltage  $V_{FS}$ .

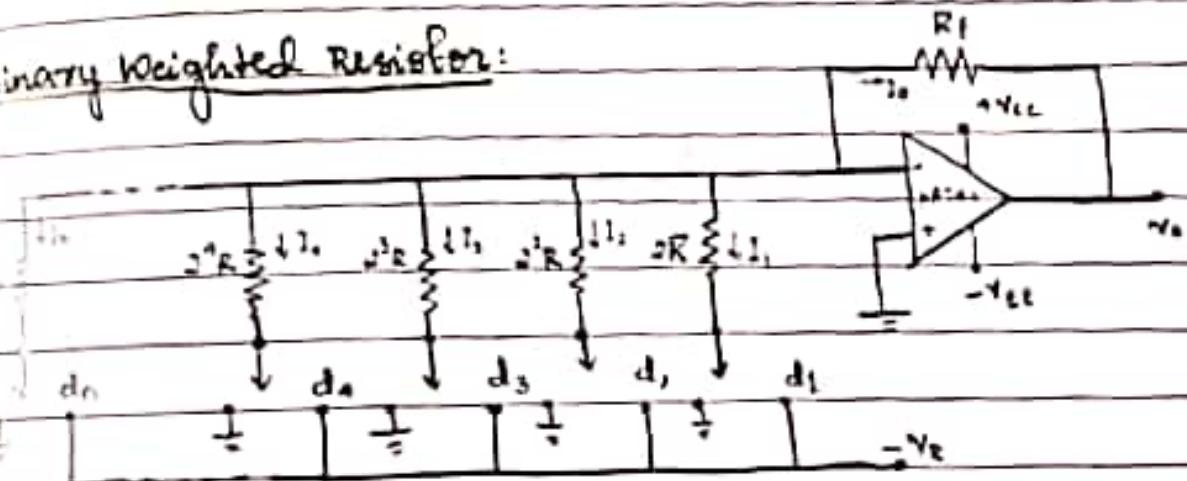Binary Weighted Resistor:

$$I_0 = I_1 + I_2 + I_3 + \dots + I_n$$

$$I_0 = \frac{V_R d_1}{2R} + \frac{V_R d_2}{2^2 R} + \frac{V_R d_3}{2^3 R} + \frac{V_R d_4}{2^4 R} + \dots + \frac{V_R d_n}{2^n R}$$

$$I_0 = \frac{V_R}{R} [2^{-1} d_1 + 2^{-2} d_2 + 2^{-3} d_3 + 2^{-4} d_4 + \dots + 2^{-n} d_n]$$


$$\text{but, } V_0 = 2k R_f$$

$$\therefore V_0 = \frac{V_R}{R} [2^{-1} d_1 + 2^{-2} d_2 + 2^{-3} d_3 + \dots + 2^{-n} d_n] R_f$$


$$\therefore V_0 = V_R [2^{-1} d_1 + 2^{-2} d_2 + 2^{-3} d_3 + \dots + 2^{-n} d_n]$$

But there will be a voltage drop across each resistor  
hence to overcome this drawback by R-2R ladder network


## 2. R-2R ladder network:

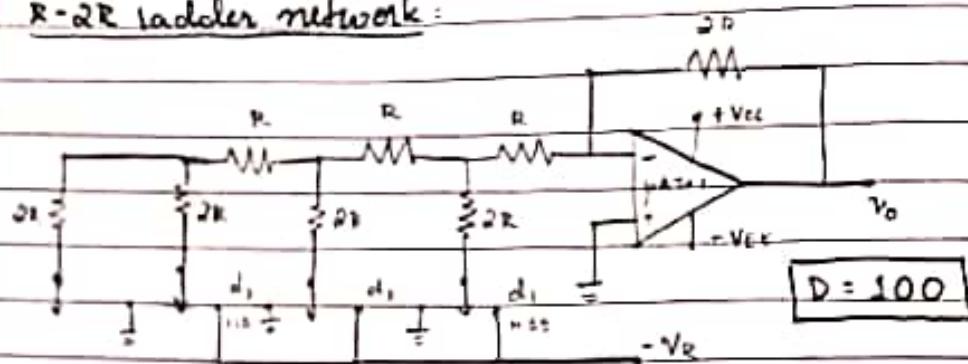

For  $D = 100$

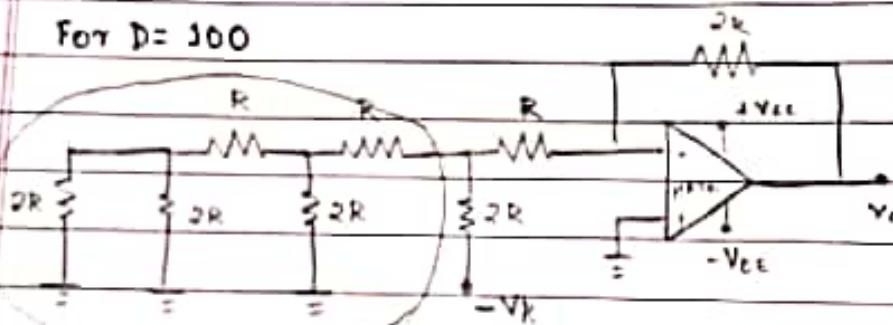


Equivalent resistance =  $2R$

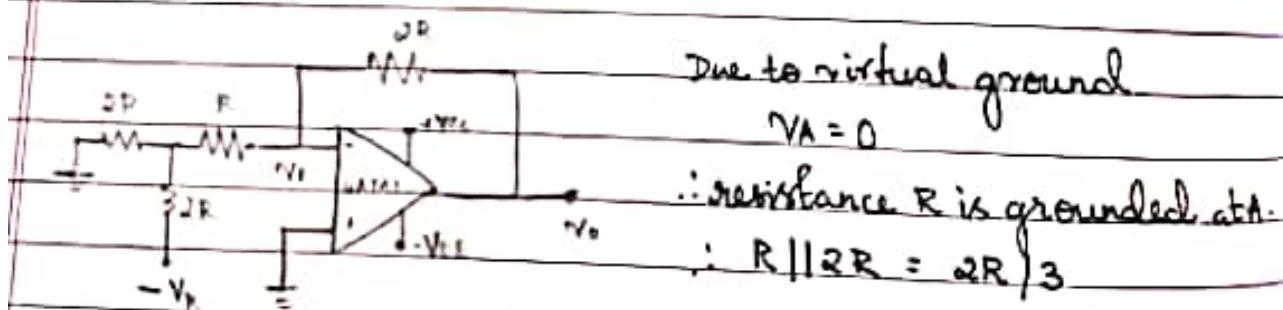

Due to virtual ground

$$V_A = 0$$

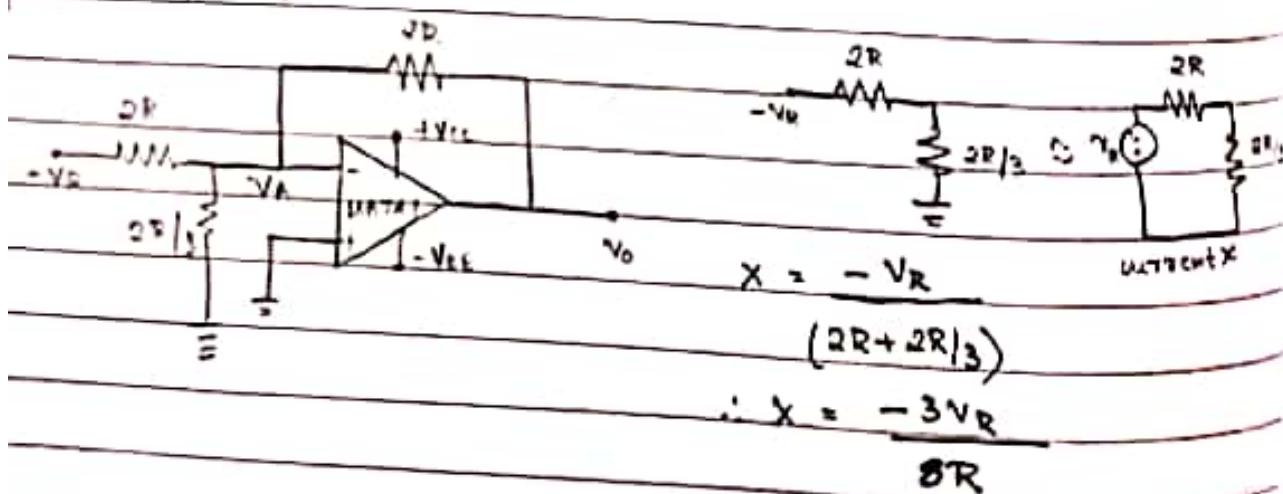$\therefore$  resistance  $R$  is grounded at  $V_A$   
 $\therefore R \parallel 2R = 2R/3$



classmate

Date \_\_\_\_\_

Page \_\_\_\_\_

Voltage at node A

$$V_A = IR$$

$$V_A = \frac{X \cdot 2R}{3}$$

$$V_A = -\frac{3V_R}{8R} \left( \frac{2R}{3} \right)$$

$$V_A = -\frac{V_R}{4}$$

For inverting amplifier

$$V_o = -\frac{R_f}{R_i} V_i$$

$$V_o = -\frac{2R}{R} \left[ -\frac{V_R}{4} \right]$$

$$\gamma_o = \frac{V_R}{2} //$$